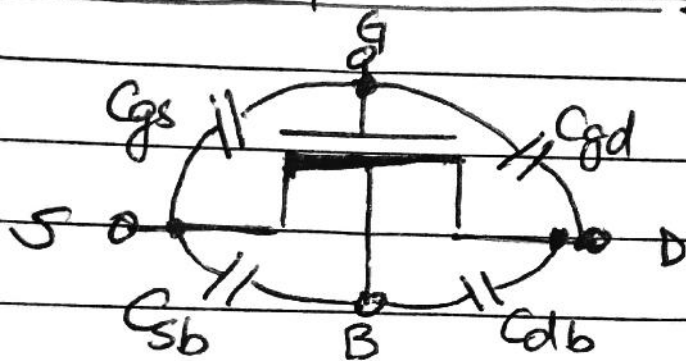


FREQUENCY RESPONSE OF TRANSISTOR CKTS

* High-Frequency ^(HF) MOS Small-Signal ^(SS) Model.

HF SS Model = LF SS Model + Parasitic Caps.

Parasitic Caps in a MOS in Saturation



where

$$C_{gs} = \frac{2}{3} WL C_{ox} + C_{ov}$$

C_{ov} is the overlap capacitance : $L_{ov} \cdot W \cdot C_{ox}$

$$C_{gd} \approx C_{ov}$$

The drain-to-bulk (C_{db}) and the source-to-bulk (C_{sb}) capacitances are depletion capacitance due to reverse biased diodes.

$$C_{sb} = (A_s + WL) C_{js} + P_s C_{jsw}$$


where A_s is the area of source junction, P_s is the effective perimeter of the source junction and C_{js} & C_{j-sw} are the area and perimeter capacitance density.

NOTE: C_{sb} includes the channel area because the channel is connected to the source junction and there is depletion underneath.


Similarly,

$$C_{db} = A_d C_{jd} + P_d C_{j-sw}$$


The HF model in the active region:

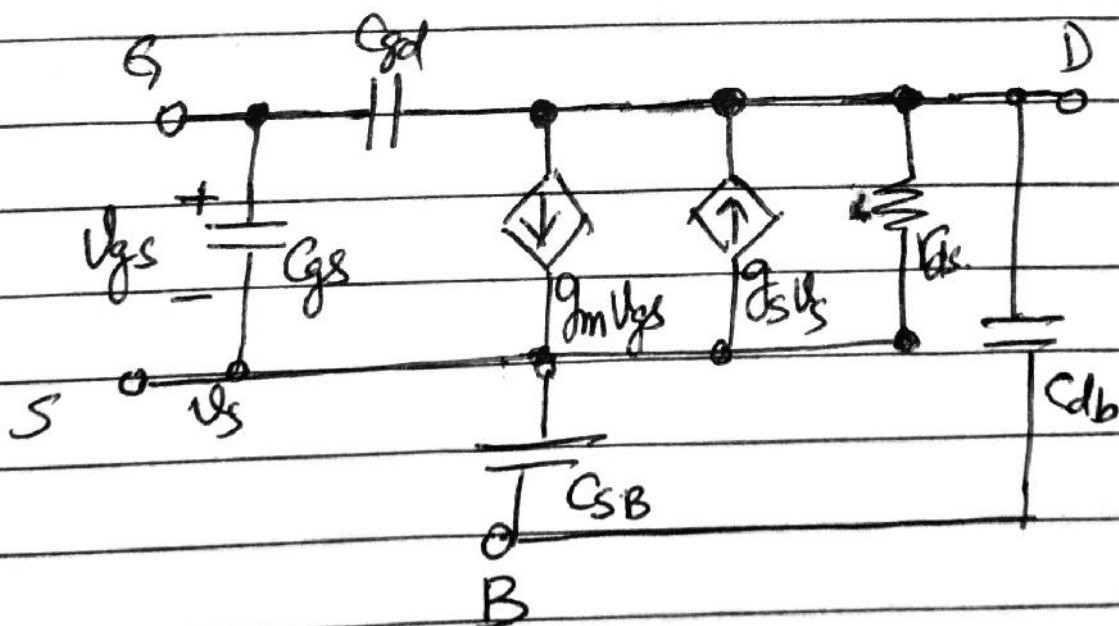

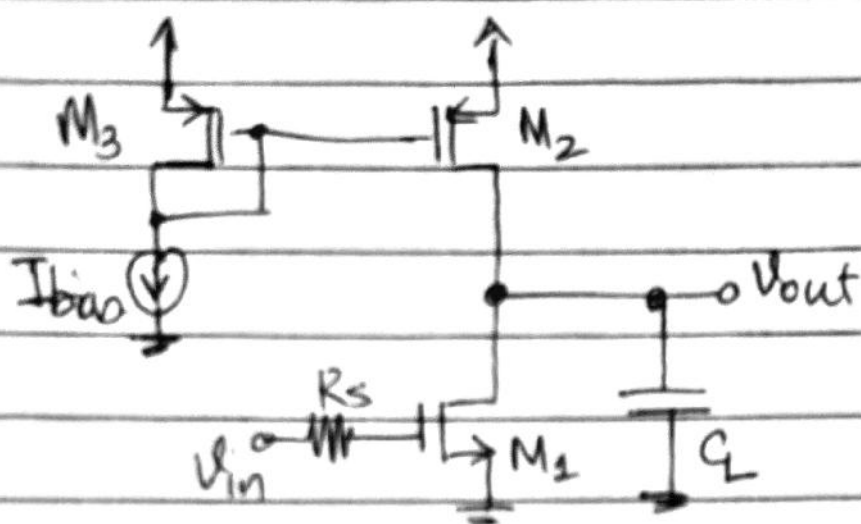FREQUENCY RESPONSE OF A COMMON-SOURCE AMPLIFIER



HF Small-signal model.

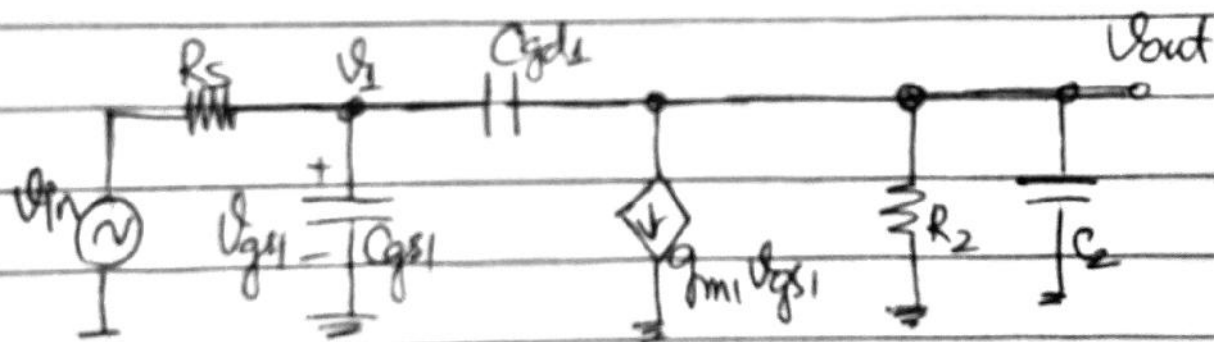

$$C_2 = C_{db1} + C_{db2} + C_{gd2} + C_L$$

$$R_2 = r_{ds1} \parallel r_{ds2}$$

Now we can ~~use~~ apply node equations as we did in resistive network by substituting the capacitors

with its equivalent Laplace impedance

KCL @ V_1

$$V_1 (G_s + sC_{gs1} + sC_{gd1}) - V_{in} G_s - V_{out} sC_{gd1} = 0 \quad \text{--- (1)}$$

KCL @ V_{out}

$$V_{out} (G_2 + sC_{gd1} + sC_2) - V_1 sC_{gd1} + g_{m1} V_1 = 0 \quad \text{--- (2)}$$

where $v_1 = v_{gs1}$

On solving (1) & (2) we get

$$A(s) = \frac{V_{out}}{V_{in}} = \frac{-g_{m1} R_2 \left(1 - s \frac{C_{gd1}}{g_{m1}} \right)}{1 + sa + s^2 b}$$

$$a = R_s [C_{gs1} + C_{gd1} (1 + g_{m1} R_2)] + R_2 (C_{gd1} + C_2)$$

&

$$b = R_s R_2 (C_{gd1} C_{gs1} + C_{gs1} C_2 + C_{gd1} C_2)$$

First sanity check for $s=0$ the result should be that of LF model.

When $s=0$ $A(s) = -g_{m1} R_2 \leftarrow$ confirmed.

Since the denominator $D(s)$ is second-order, it has two poles. and if assume they are far apart ie. $\omega_{p1} \ll \omega_{p2}$, the denominator can be expressed as

$$D(s) = \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right) \approx 1 + \frac{s}{\omega_{p1}} + \frac{s^2}{\omega_{p1}\omega_{p2}}$$

then

$$\omega_{p1} \approx \frac{1}{a} = \frac{1}{R_S [C_{gs1} + \underbrace{C_{gd1}(1+g_{m1}R_2)}_{\text{Miller Cap.}}] + R_2 (\underbrace{C_{gd1} + C_2}_{\text{Typically dominant.}})}$$

$$\omega_{p2} \approx \frac{1}{\omega_{p1} b} \approx \frac{g_{m1} C_{gd1}}{C_{gs1} C_{gd1} + C_{gs1} C_2 + C_{gd1} C_2}$$

And the high frequency zero

$$\omega_z = -g_{m1}/C_{gd1}$$

Since $\omega_{p1} \ll \omega_{p2}, \omega_z$, a dominant-pole approximation may be applied for frequencies $\omega \ll \omega_{p2}, \omega_z$

$$A(s) \approx A_0 = \frac{-g_m R_2}{1 + \frac{s}{\omega_{p1}}}$$

For special case where the load capacitance and therefore C_2 is large;

$$\omega_{p1} \approx \frac{1}{R_2 C_2}$$

$$\omega_{p2} \approx \frac{C_{gd1}}{C_{gs1} + C_{gd1}} \cdot \frac{g_{m1}}{C_2}$$

BODE PLOTS

Once the s -domain transfer function is formulated, plotting the transfer function versus frequency is an essential analytic tool.

If we consider the transfer function of the previous example with two widely separated poles:

$\downarrow \omega_{p1} \ll \omega_{p2}$ / real poles.

$$A(s) = \frac{A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}$$

where A_0 is the DC ($\omega=0$) gain
i.e. $A_0 = -g_m R_2$

Since $A(s)$ is a complex number, the transfer function is analyzed by plotting both Magnitude $|A(j\omega)|$ & the Phase $\angle A(j\omega)$.

With the assumption of widely separated poles, the magnitude & phase can be plotted for different ~~for~~ frequency regions.

(1) For $\omega \ll \omega_{p1}$, $A(j\omega) = -A_0$
or $A(j\omega) = -g_m R_2$

or $|A(\omega)| = -g_m R_2$ or $g_m R_2$
& $\angle A(\omega) = 0^\circ$ 180°

(2) At $\omega = \omega_{p1}$, $|A(\omega)| = \frac{g_m R_2}{\sqrt{2}}$
 $\angle A(\omega) = -180^\circ - 45^\circ$

(3) For $\omega_{p1} \ll \omega \ll \omega_{p2}$

$$|A(\omega)| \approx \frac{g_m R_2 \cdot \omega_{p1}}{\omega}$$

If we express the magnitude in decibels (dB)

$$|A(\omega)|_{dB} \approx 20 \log(g_m R_2 \cdot \omega_{p1}) - 20 \log(\omega)$$

Thus the magnitude response is decreasing -20 dB for every decade increase in ω or known as 20 dB-per-decade

In addition, in this region, we have $\angle A(\omega) \approx -180^\circ - 90^\circ = -270^\circ$.

④ $\omega = \omega_{p2}$

$$|A(\omega_{p2})| = \frac{g_m R_2 \cdot \omega_{p1}}{\sqrt{2} \cdot \omega_{p2}}$$

$$\angle A(\omega_{p2}) = -180^\circ - 135^\circ$$

⑤ Finally for $\omega \gg \omega_{p2}$

$$|A(\omega)| = \frac{g_m R_2 \cdot \omega_{p1} \cdot \omega_{p2}}{\omega^2}$$

$$\text{In dB, } |A(\omega)|_{\text{dB}} \approx 20 \log(g_m R_2 \cdot \omega_{p1} \cdot \omega_{p2}) - 40 \log(\omega)$$

\Rightarrow 40 dB-per-decade fall

$$\angle A(\omega) = -180^\circ - 180^\circ$$

THE PLOT

