
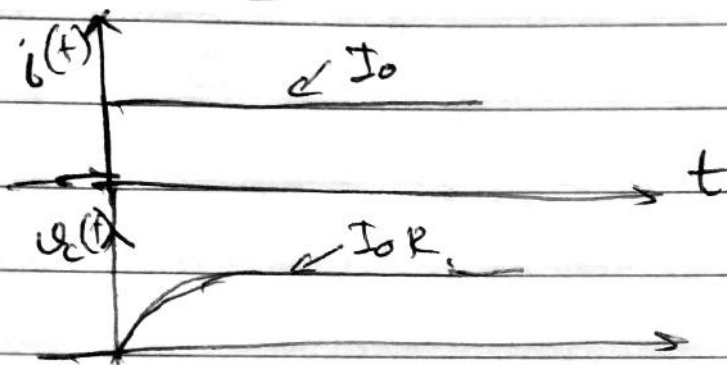


DYNAMIC CIRCUIT ANALYSIS

PARALLEL RC CIRCUIT, STEP INPUT

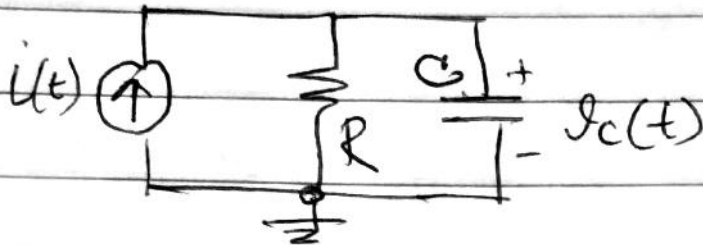

Node Analysis results in

$$i(t) = \frac{v_c}{R} + C \frac{dv_c}{dt}$$

Or, re writing,

$$\frac{dv_c}{dt} + \frac{v_c}{RC} = \frac{i(t)}{C}$$

~~Linear~~ Linear diff eqn with constant coeff.

Solution contains two parts:

- 1) homogenous solution &
- 2) particular solution

The complete solution is the summation of two

Homogenous solution:

$$\frac{dV_{CH}}{dt} + \frac{V_{CH}}{RC} = 0$$

Choosing $V_{CH} = Ae^{st}$ & substituting
~~the~~ above & solving we get

$$s = -1/RC \quad \leftarrow \text{characteristic eqn.}$$

$\therefore V_{CH} = Ae^{-t/RC}$ \leftarrow dimension of time
called the time constant.

Particular solution

$$I_0 = \frac{V_{CP}}{R} + C \frac{dV_{CP}}{dt}$$

$\therefore I_0$ is constant for $t > 0$, one
acceptable solution:

$$V_{CP} = K$$

On substituting in above eqn.:

$$V_{CP} = I_0 R$$


∴ Complete solution is

$$V_C = A e^{-t/RC} + I_0 R$$

A is derived from initial cond. at $t=0$
 $\Rightarrow A = -I_0 R$

$$\therefore V_C = -I_0 R e^{-t/RC} + I_0 R$$

$$\boxed{V_C = I_0 R (1 - e^{-t/RC})}$$

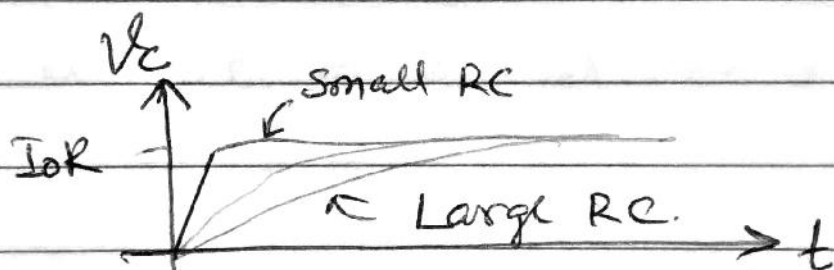


Discharge Transient

— Homogenous solution with
initial condition $V_C = I_0 R$,

$$\Rightarrow V_{CH} = A e^{-t/RC}$$

∴ $V_{CH} = I_0 R$ when $t=0$

$$\boxed{V_C = I_0 R \cdot e^{-t/RC}}$$

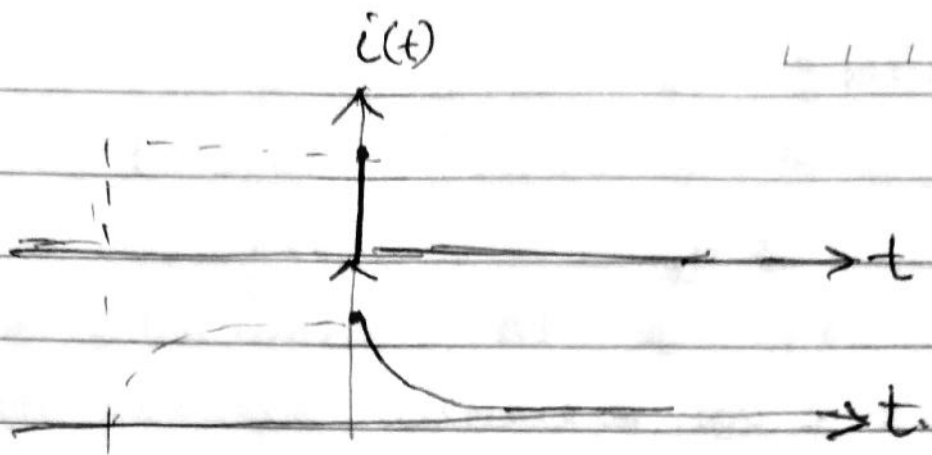

General form:


$$v_c = v_c(0) e^{-t/RC}$$

Some properties of $e^{-t/RC}$

► For $x = Ae^{-t/RC}$

the initial slope at $t=0$

$$\left. \frac{dx}{dt} \right|_{t=0} = -\frac{A}{\tau}$$

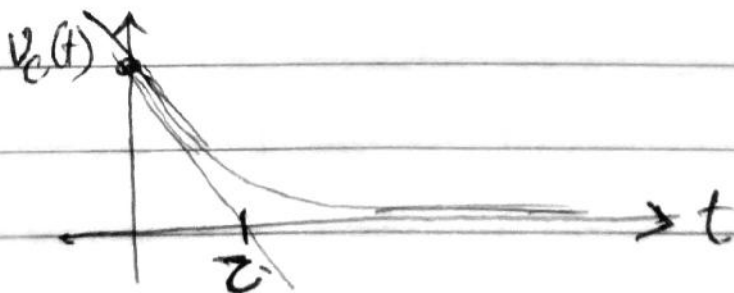

► At $t = \tau$, $x(t = \tau) = \frac{A}{e}$

$$\star t_{90\%} - t_{10\%} = RC \ln\left(\frac{0.9}{0.1}\right) = \underline{\underline{2.22}}$$

► At $t = 5\tau$ $x(5\tau) = \frac{A}{e^5} \approx 0.006A$

In other words, at $t = 5\tau$, the output is assumed to be fully settled in steady state.


Similar Analysis can be made for the Thevenin equivalent.

So for a square-wave input, the two conditional analysis results can be used.

REVIEW IC DEVICES

Diode:


heavily doped

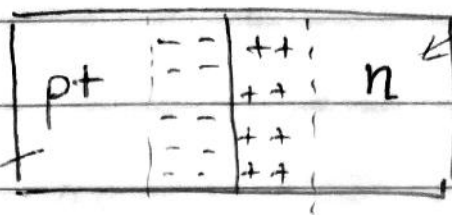

mildly doped


$$I_D \approx I_S e^{V_D/V_T} \leftarrow kT/q$$
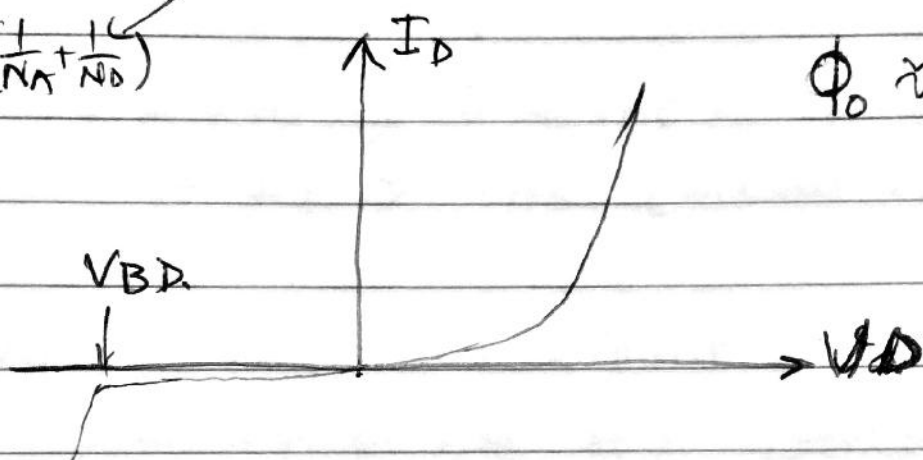
$$\propto A_d \left(\frac{1}{N_A} + \frac{1}{N_D} \right)$$



$$\phi_0 \approx 0.9V$$

Reverse bias junction Capacitance.

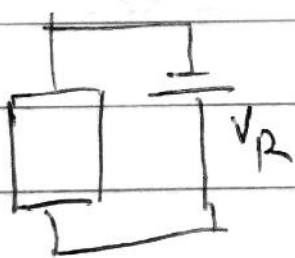



$$C_j = \frac{C_{j0}}{\sqrt{1 + V_R/\phi_0}} \leftarrow \text{non-linear}$$

\uparrow
 $\rightarrow f(V_R)$

When switching between V_1 & V_2
it can be approximated with

$$C_{j-av} = \frac{2C_{j0}\phi_0 [\sqrt{1+V_2/\phi_0} - \sqrt{1+V_1/\phi_0}]}{V_2 - V_1}$$

MOS BIASING & OPERATION

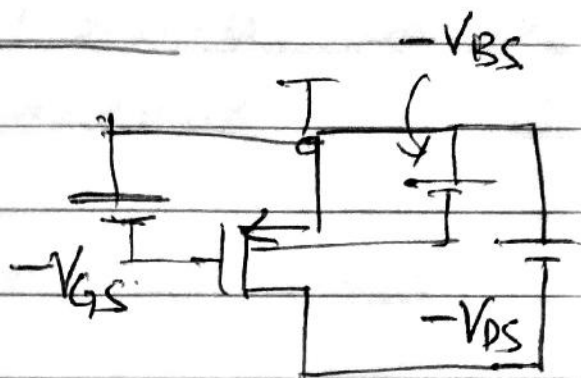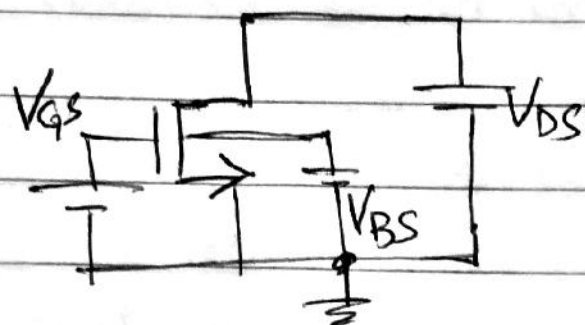

* $V_{GS} > V_{TO}$, $0 < V_{DS} < V_{DSat}$
 $-I_D \propto V_{DS}$ [Linear region]

* $V_{GS} > V_{TO}$, $V_{DS} > V_{DSat}$
 $-I_D \propto (V_{GS} - V_T)^2$ [Saturation region]

* $V_{GS} < V_{TO}$
 — Subthreshold region OR cut-off
 $I_D \propto e^{V_{GS}}$ $I_D \approx 0$

To determine if it's in subthreshold we need to know the inversion coefficient IC given by

$$IC = I_D / I_S$$

where $I_S = \frac{2\mu C_{ox} V_T^2}{K} \cdot \frac{W}{L}$

where,
 $V_T = kT/q$
 $K \propto 0.7$


For $I_C < 0.1$, it's in weak inversion or sub-threshold operation

Moderate Inversion: $0.1 < I_C < 10$

Strong Inversion: $I_C > 10$

g_m/I_D is more appropriate design parameter to be discussed later.

Large-Signal I_D - V_{DS} Response

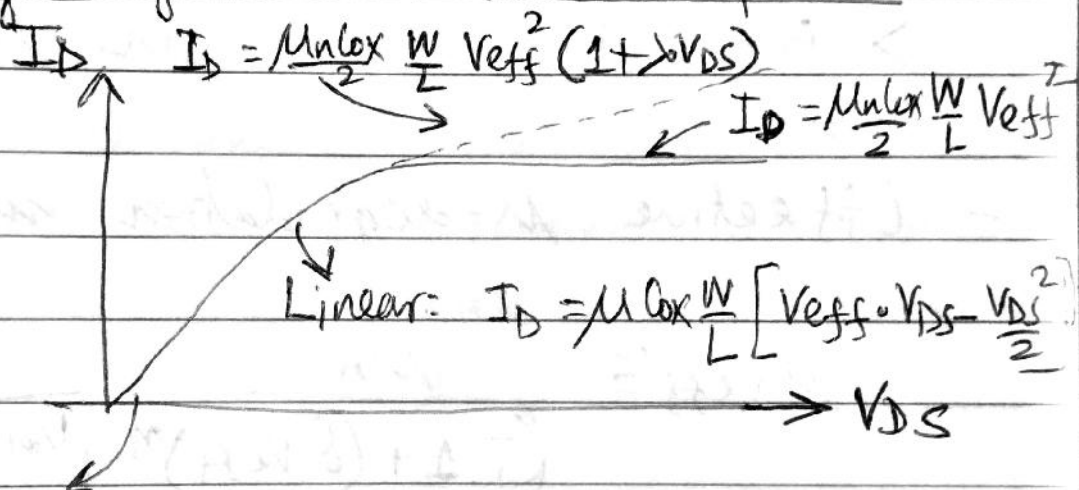

$$I_D \approx \mu C_{ox} \frac{W}{L} (V_{GS} - V_{th}) V_{DS}$$

Linear resistor $R_{on} = \frac{V_{DS}}{I_D} = \frac{1}{\mu C_{ox} \frac{W}{L} V_{eff}}$

$\mu \rightarrow$ mobility of the channel

$\lambda \rightarrow$ channel length modulation coefficient

$V_{eff} \rightarrow V_{GS} - V_T \Rightarrow$ excess bias

also written as V_{on} , V_{sat}

98, 138, 348

~~When~~

When $0.1 < IC < 10$ both

strong & weak inversion expression over estimate g_m .

Accurate expression is using EKV.

$$g_m \approx \frac{K I_D}{U_T} \cdot \frac{2}{1 + \sqrt{1 + 4 \cdot IC}}$$

The current mechanism in subthreshold region is diffusion since channel is not formed.

$$I_D \approx I_{D0} \left(\frac{W}{L} \right) e^{\left(q V_{gs} / n k T \right)}$$

$$n = \frac{C_{ox} + C_{go}}{C_{ox}} \approx 1.5$$

$$I_{D0} = (n-1) \mu_n C_{ox} \left(\frac{kT}{q} \right)^2$$

BODY EFFECT

In the previous sections, the large signal equations are valid under the assumption that the source & bulk are at the same potential i.e. $V_{SB} = 0V$.

However, often case, that is not the case.

Typically called the body effect, the influence of the body potential on the channel is modelled as an increase in the threshold voltage, V_{tn} , with increasing source-to-body bias. For a NMOS,

$$V_{tn} = V_{tn0} + \gamma \cdot (\sqrt{V_{SB} + 2|\phi_F|} - \sqrt{2|\phi_F|})$$

$$\text{where, } \phi_F = \frac{KT}{q} \ln(N_A/n_i), \quad \gamma = \frac{\sqrt{2qNAK_s\epsilon_0}}{C_{ox}}$$

Short-channel effects

Mobility degradation

- Large electric field \rightarrow effective mobility degradation
- Velocity saturation $\sim 10^7$ cm/s due to high lateral E -field
- In addition, vertical E -field $> 5 \times 10^6$ V/m result in μ -degradation
- Effective μ -degradation model:

$$\mu_{n\text{eff}} \approx \frac{\mu_n}{\left[1 + (\theta V_{\text{eff}})^m\right]^{1/m}}$$

$\theta, m \rightarrow$ device parameters

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{\text{eff}}^2 \left[\frac{1}{1 + (\theta V_{\text{eff}})^m} \right]^{1/m}$$

Short channel effects: Hot Carrier

- High velocity electrons near the drain cause electron-hole pair leading to substrate current
- results in low output impedance & therefore problem in using them for current mirrors.
- another effect is the hot carriers entering the oxide & causing finite gate current.
- Causes shift in threshold voltage & reliability.