

Problem 8.3


0.35 μm nMOS

$$\mu_{n\text{ox}} = 190 \frac{\mu\text{A}}{\text{V}^2}$$

$$\lambda \cdot L = 0.16$$

$$C_{\text{ox}} = 4.5 \text{ fF}/\mu\text{m}^2$$

$$V_{\text{eff}2} = 205 \text{ mV}$$

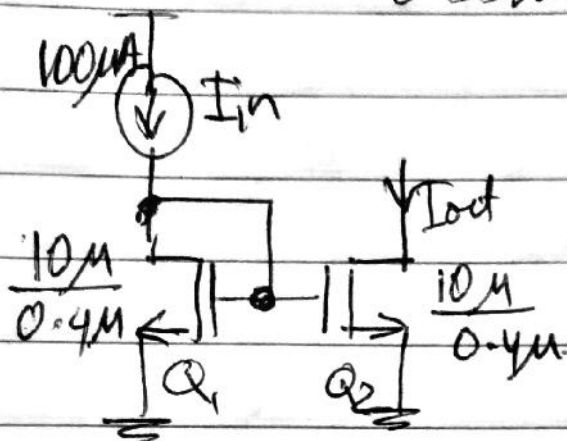

- Find resulting change in I_{out} for
- threshold voltage of Q_2 increase by 5 mV
 - μ_n of Q_2 increases by 5%
 - L_2 increases to 0.42 μm .

Solution:

$$(a) I_{\text{out}}' = \frac{\mu_{n\text{ox}}}{2} \frac{W}{L} (V_{\text{eff}} + \Delta V_{\text{th}})^2$$

$$= I_{\text{out}} \left(1 + \frac{\Delta V_{\text{th}}}{V_{\text{eff}}} \right)^2$$

$$\approx I_{\text{out}} \left(1 + \frac{2\Delta V_{\text{th}}}{V_{\text{eff}}} \right) = 1.05 \cdot I_{\text{out}}$$

$$= \underline{\underline{105 \mu\text{A}}}$$

5% error.

$$(b) I_{out}' = \frac{1.05 \mu_n C_{ox}}{2} \frac{W}{L} (V_{eff2})^2$$

$$= 1.05 I_{out}$$

$$I_{out}' = 105 \mu A \quad \pm 5\% \text{ error.}$$



$$(c) I_{out}' = \frac{\mu_n C_{ox}}{2} \frac{W}{L(1+0.05)} V_{eff}^2$$

Using Taylor expansion of $\frac{1}{1+\Delta x} \approx 1-\Delta x$

$$\therefore I_{out}' \approx (1-0.05) I_{out} = 95 \mu A$$

\therefore 5% error in I_{out} for 5% error in L

CASCODE CURRENT MIRROR

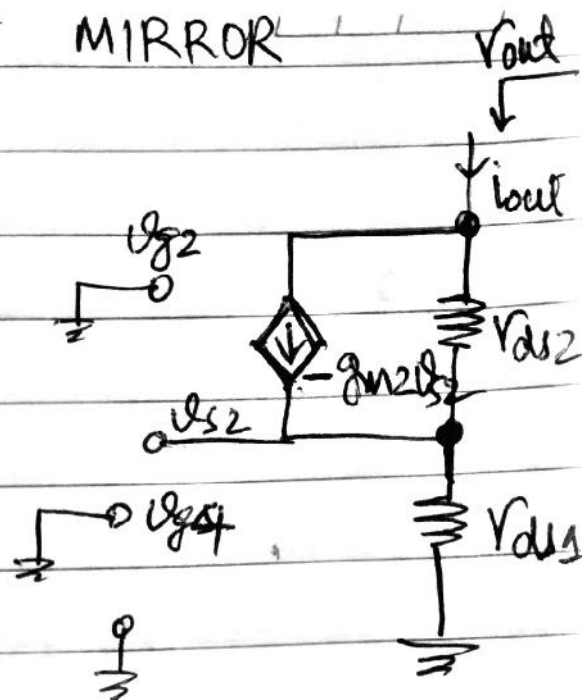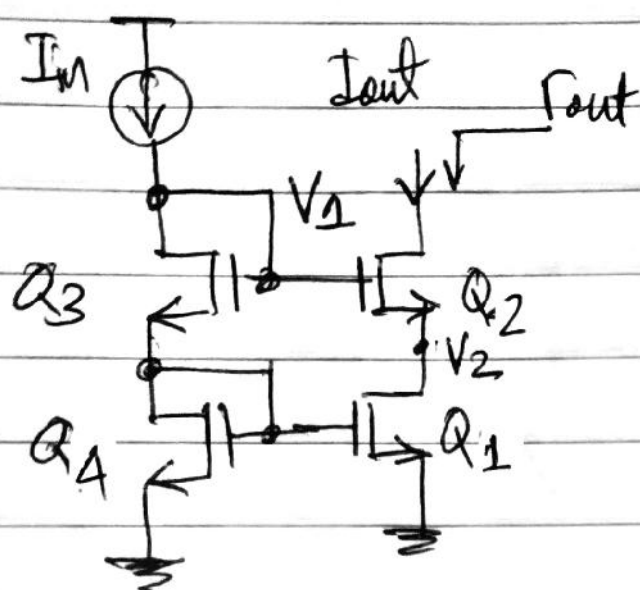

Based on our result from source degeneration CM we can write

$$r_{out} \approx r_{ds2} (1 + g_{m2} \cdot r_{ds1})$$

Compliance:

Assuming all transistors identical

$$V_1 = 2V_{GS}$$

$$V_2 = V_1 - V_{GS} = V_{GS}$$

$$\therefore V_0(\min) = V_2 + V_{eff2} = V_{th} + 2V_{eff}$$

$\underbrace{\hspace{1cm}}$
 wasted headroom.

P 3.20

0.35 μm CMOS: $\lambda \cdot L = 0.16 \frac{\mu\text{m}}{\text{V}}$


$$I_{in} = 300 \mu\text{A}$$

$$\left(\frac{W}{L}\right)_{1,2,3,4} = \frac{50 \mu\text{m}}{0.5 \mu\text{m}}, \quad V_{tn} = 0.57$$

$$V_{eff\ 1,2,3,4} = \sqrt{\frac{2 \times 300 \mu\text{A}}{190 \mu\text{A} \frac{50}{\sqrt{2} \cdot 0.5}}} = 177 \text{ mV}$$

$$V_o(\text{min}) = \underbrace{V_{tn}}_{\text{costly}} + 2V_{eff} = \underline{\underline{0.924 \text{ V}}}$$

Output Impedance:

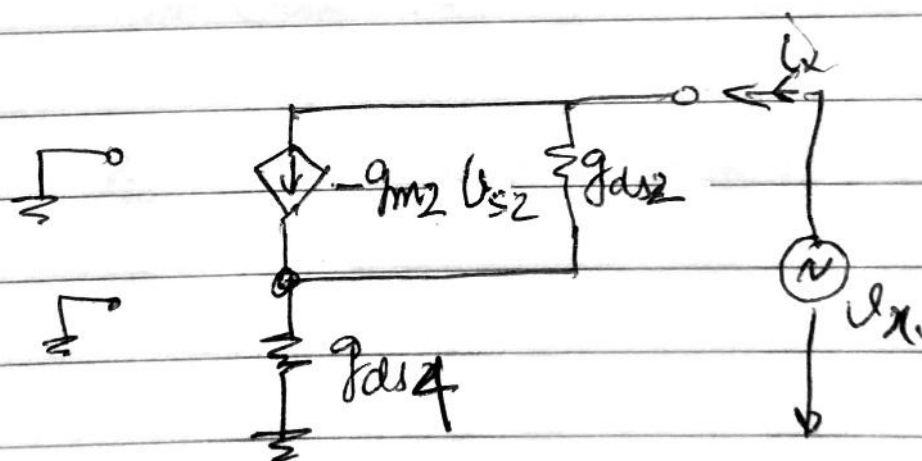


$$r_{ds2} = r_{ds4} = \frac{1}{\lambda \cdot I_D} = \frac{0.5 \mu\text{m}}{0.16 \times 300 \mu\text{A}} = 10.41 \text{ k}\Omega$$

$$g_{m2} = \frac{2I_D}{V_{eff}} = \frac{2 \times 300 \mu\text{A}}{0.177 \text{ V}} = 3.38 \text{ mS}$$

$$R_{out} \approx 10.41 \text{ k} (1 + 3.38 \text{ m} \times 10.41 \text{ k}) = \underline{\underline{376.69 \text{ k}}}$$

36x improvement !!

PROBLEM 8.40

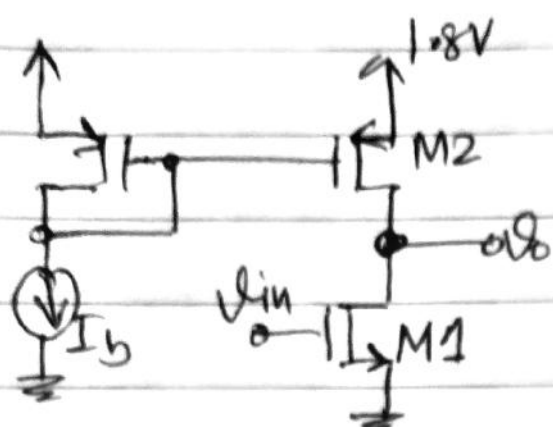

Technology: $0.18\mu\text{m CMOS}$

Power = 1mW

$V_{eff1,2} = 250\text{mV}$

$L = 0.25\mu\text{m}$

Gain > 5

$\mu_n C_{ox} = 270\mu\text{A/V}^2$, $\mu_p C_{ox} = 70\mu\text{A/V}^2$

For 1mW power: $1.8\text{V} \times I_{D1} = 1\text{mW}$

$$\Rightarrow I_{D1} = I_{D2} = 555\mu\text{A}$$

$$V_{ds1} = V_{ds2} = \frac{1}{\lambda I_D} = \frac{0.25\mu}{0.08\frac{\text{mV}}{\text{V}} 555\mu\text{A}} = 5.6\text{k}\Omega$$


$$v_o \text{ gain} = g_{m1} (V_{ds1} \parallel V_{ds2}) = \frac{2I_D}{V_{eff}} \times \left(\frac{5.6\text{k}}{2} \right)$$

$$= \frac{2 \times 555\mu}{0.25\text{V}} \times 2.8\text{k} = 24.8 > 5$$

$$\frac{W_1}{L_1} = \frac{I_{D1} \times 2}{\mu_n C_{ox} (0.25)^2} \approx 65$$


$$\frac{W_2}{L_2} = \frac{I_{D1} \times 2}{\mu_p C_{ox} (0.25)^2} = 253$$

WIDE SWING CURRENT MIRROR

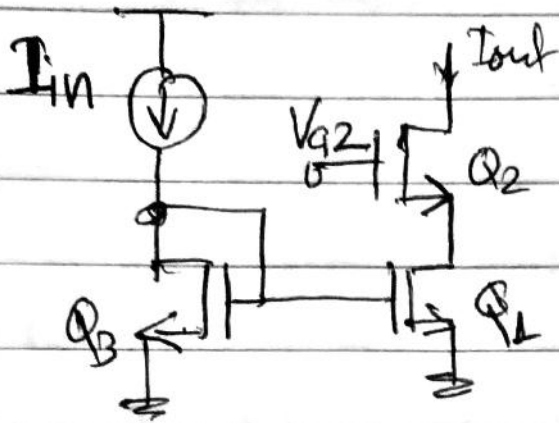


$$V_{G2}(\min) = V_{DS1}(\min) + V_{GS2}$$

$$= V_{EFF1} + V_{GS2}$$

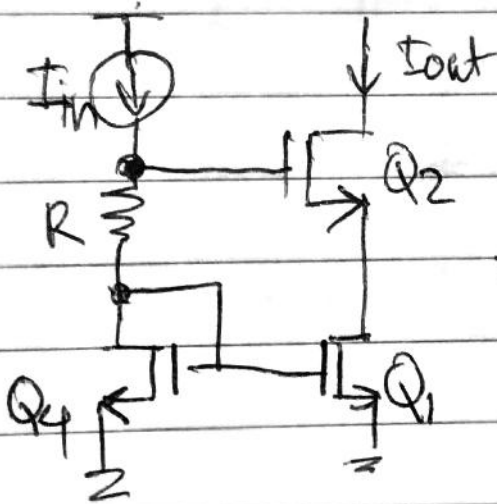

To keep
 $V_{DS1} = V_{DS2}$

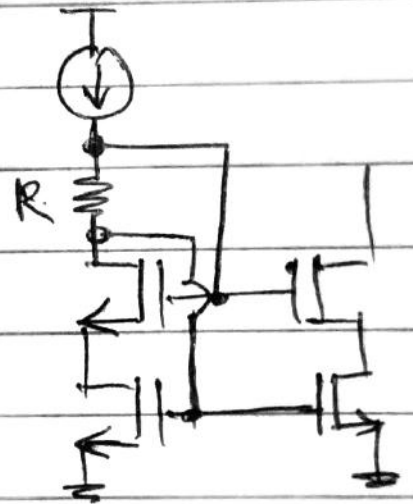


Choose R such that $I_{in}R = V_{DS1}$

An example:

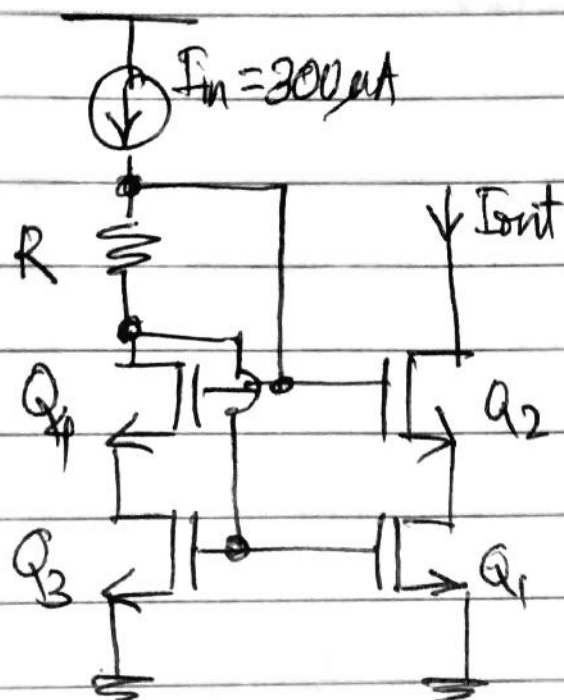0.35 μm CMOS

$$(W/L)_{1,2,3,4} = \frac{50 \mu\text{m}}{0.5 \mu\text{m}}$$



$$V_{th} = 0.57 \text{ V}, V_{eff} = 177 \text{ mV}$$


$$\therefore \text{Choose } R = \frac{177 \text{ mV}}{300 \mu\text{A}}$$

$$= 590 \Omega$$


$$V_{DS1} = V_{GS3} + I_n R - V_{GS2} = 177 \text{ mV} < V_{eff1}$$

$$V_o(\text{min}) = V_{DS1} + V_{eff2} = 2 \cdot V_{eff} = \underline{\underline{0.354 \text{ V}}}$$

COMMON-SOURCE AMP WITH CASCODE LOADS

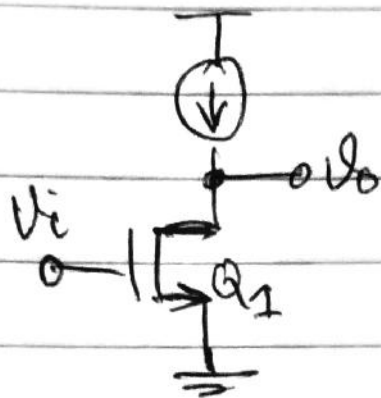

$$A_v \approx g_{m1} \cdot r_{ds1}$$

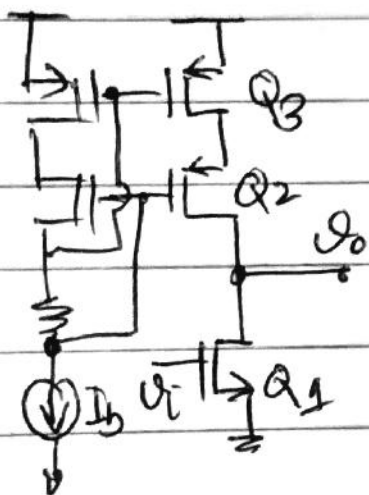

$$A_v \approx g_{m1} \cdot r_{ds1} \parallel \left[r_{ds2} (1 + g_{m2} r_{ds3}) \right]$$

small \parallel big
small

