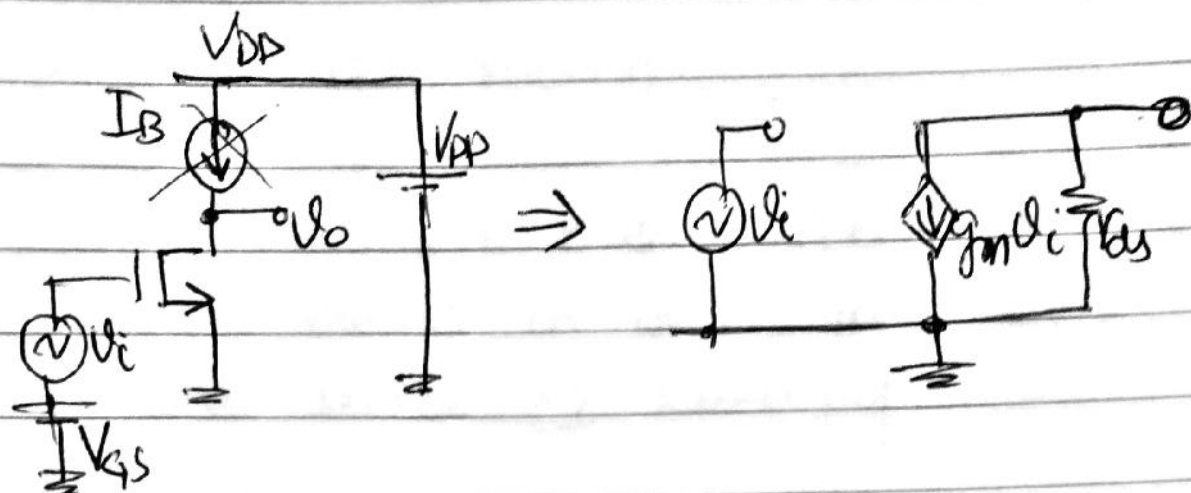


RECAP : SMALL-SIGNAL MODELING



- Set all AC (small-signal) independent sources to zero : $\circ \rightarrow$ open, $i \rightarrow$ short
- Find the DC operating point (g_m, g_{ds})
- Set all the DC (Bias) independent sources to zero
- Replace all non-linear elements with their small-signal equivalent.
- Calculate the small-signal response.


CURRENT MIRRORS

Why current mirrors?

→ Provide bias current for multiple blocks in an IC from one single pristine source eg. Bandgap reference.

→ Active load for amplifiers.


BIAS CIRCUIT FOR DISCRETE MOS

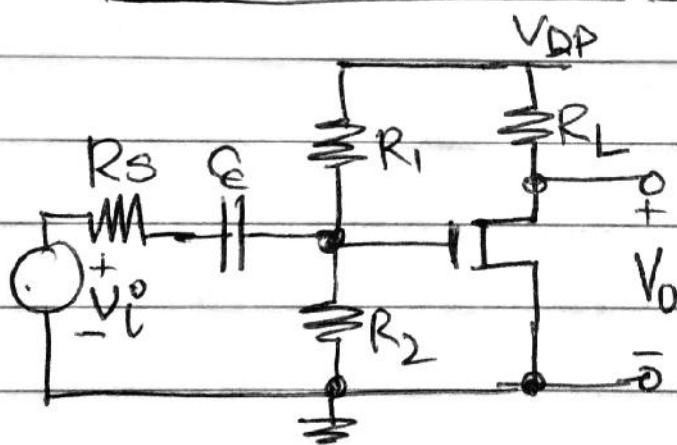

Not suitable for IC:


- Resistors consume big area.
- C also big area
- Bias current variations huge.

Current Mirrors as bias currents

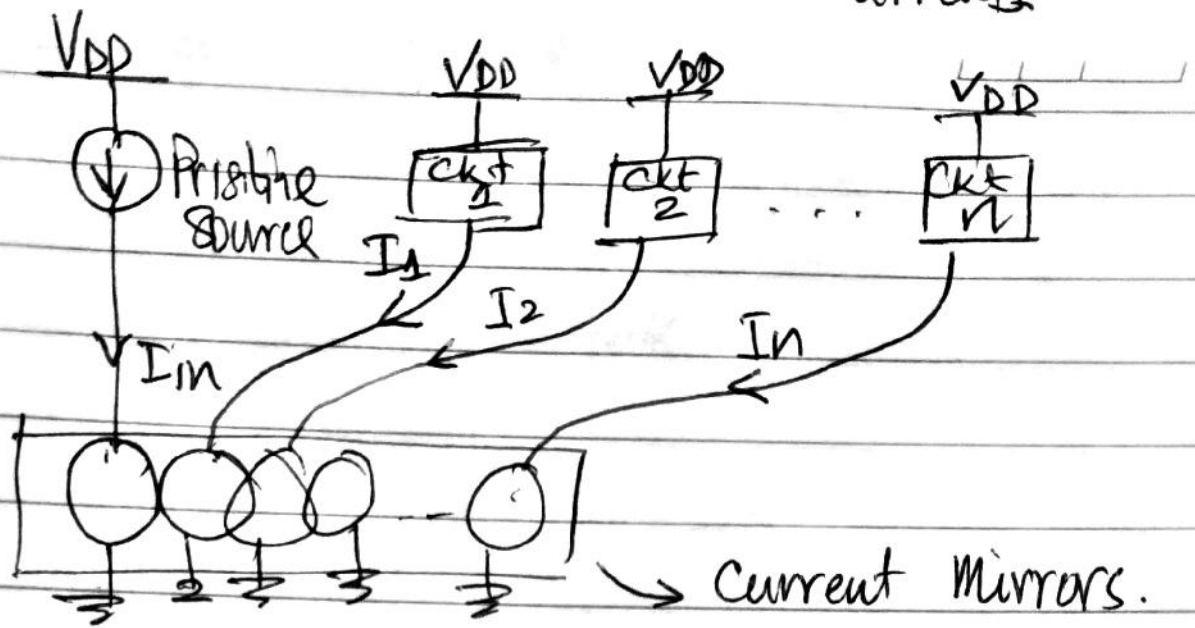


Why Active Load?


P 1.19

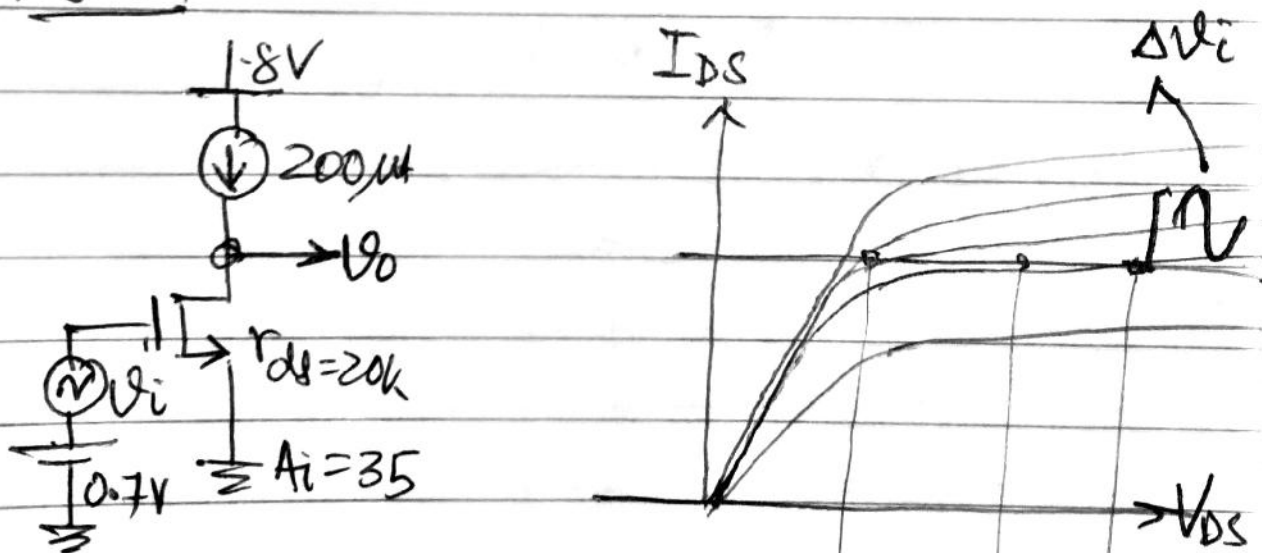

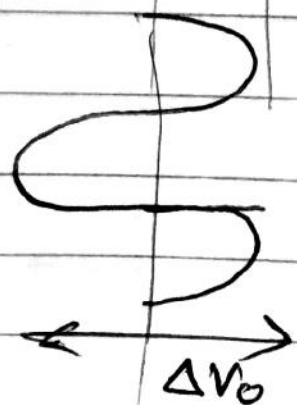
→ Key: Bias current is independent of output impedance



Resistive Load.

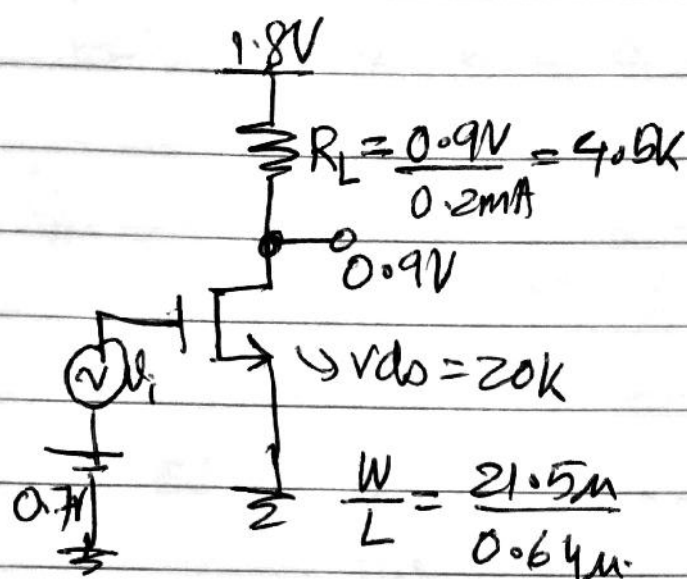
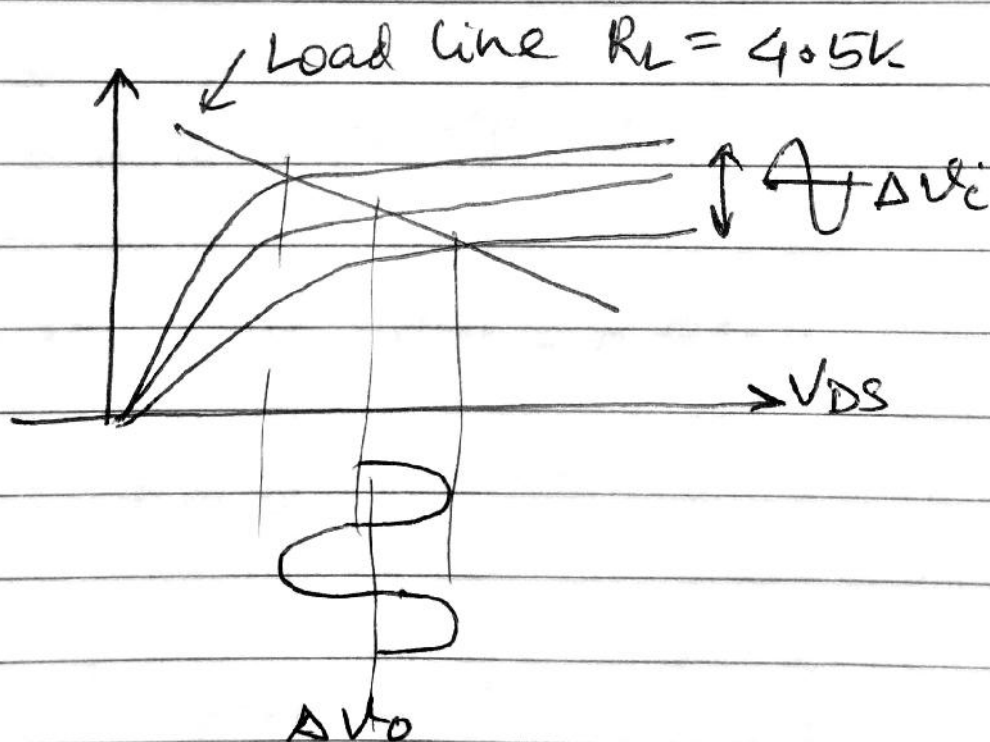
$$A = g_m \times (r_{ds} \parallel R_L) \approx g_m R_L = 28.$$




% Bias current and output impedance are NOT independent.

How to Create Current Mirrors

Let's say we want $80\mu\text{A}$.

Eg. NMOS biased in saturation is a current mirror.

$0.8\mu\text{m NMOS}$

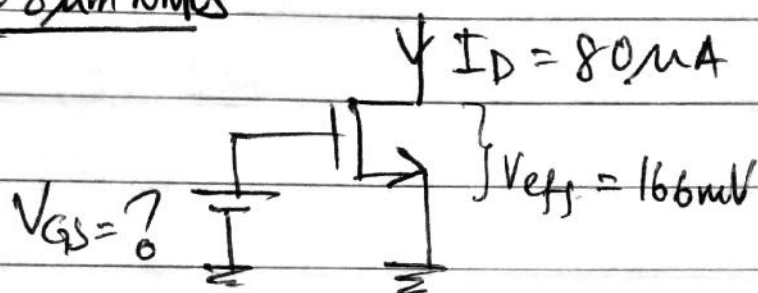


$$\begin{aligned} \beta &= \mu_{n\text{ox}} = 92 \frac{\mu\text{A}}{\text{V}^2} \\ V_{tn} &= 0.8\text{V} \\ \frac{W}{L} &= \frac{100\mu}{1.6\mu} \end{aligned}$$

$$I_D = \frac{\mu_{n\text{ox}}}{2} \cdot \frac{W}{L} V_{eff}^2 \Rightarrow V_{eff} = \sqrt{\frac{2I_D}{\mu_{n\text{ox}} W/L}} = 0.166\text{V}$$

$$\therefore V_{GS} = V_T + V_{eff} = 0.966\text{V}$$

& $V_{DS} > V_{eff}$.

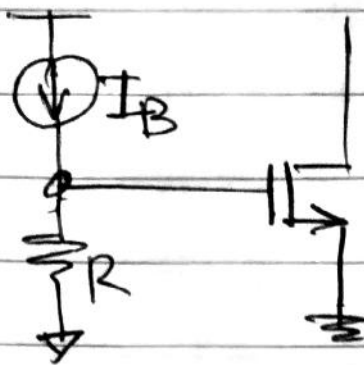How to generate 0.966V from
the $80\mu\text{A}$



$$80 \mu\text{A} \cdot R = 0.966 \text{V}$$


$$\Rightarrow R = \frac{0.966 \text{V}}{80 \mu\text{A}} \approx 12 \text{k}\Omega$$

$$I_B \cdot R = V_{GS} \quad ?$$


Two reasons this not preferable

- ① Large area for the resistor
- ② Large variation due to Process, Temp


Better way:

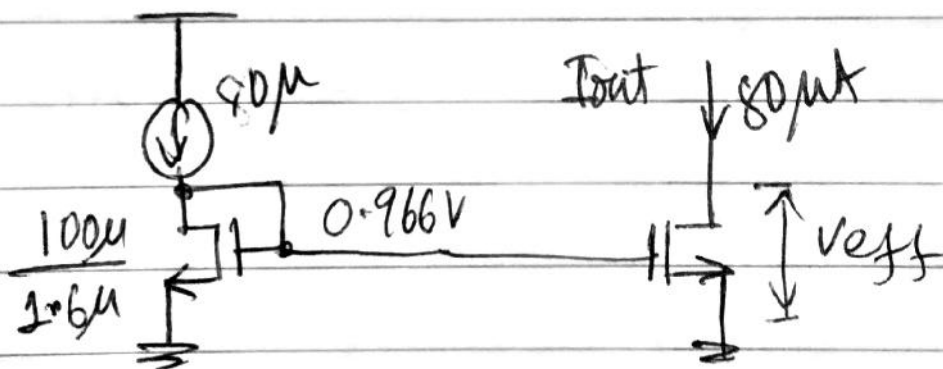

Voltage Compliance

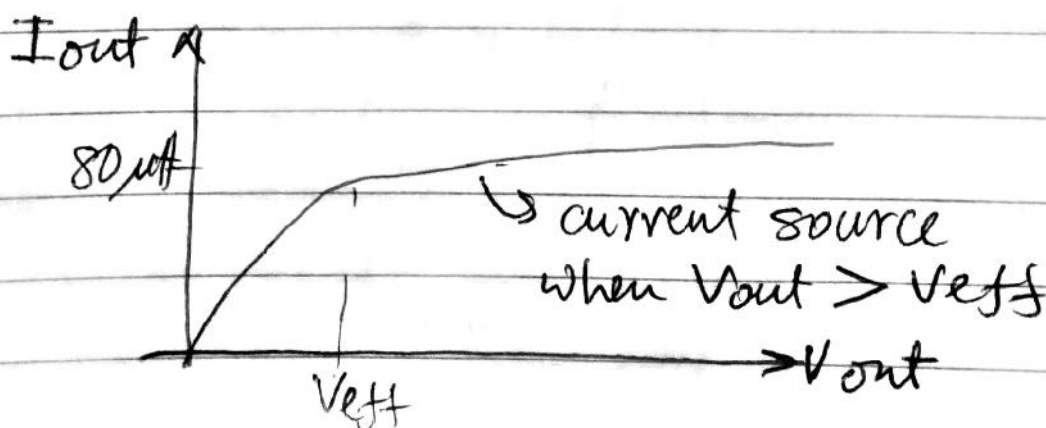

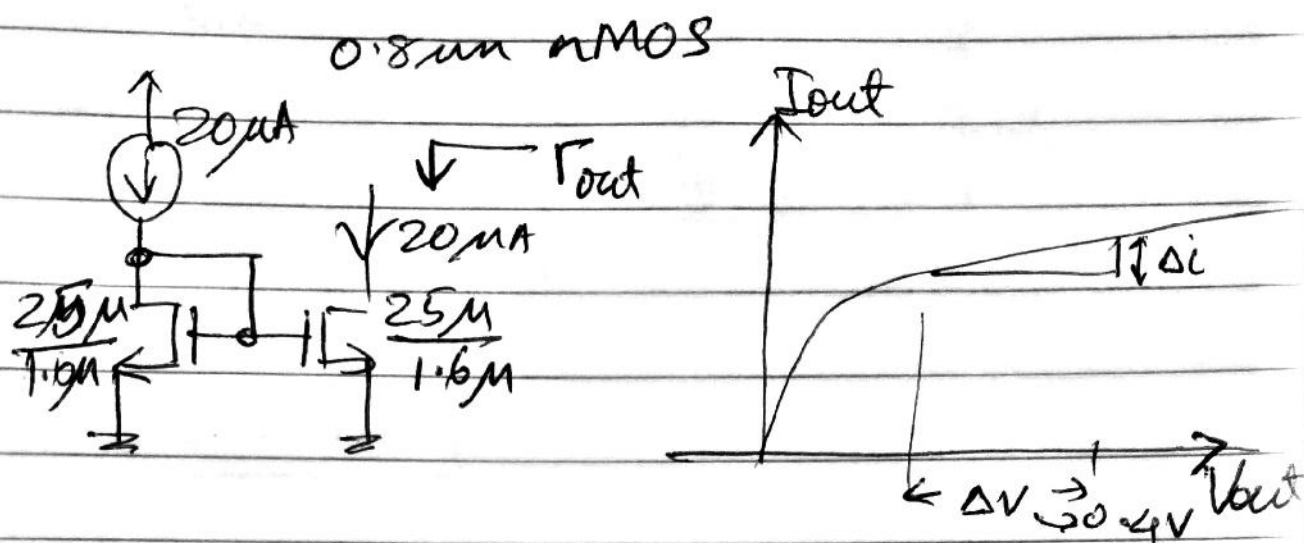Error in Output current
due to finite ^{out} impedance.




$$\lambda \cdot L = 0.12 \mu\text{m/V} \quad r_{ds} \approx \frac{1}{\lambda I_d} = 666 \text{ k}\Omega$$


$$\Delta I \approx \frac{\Delta V}{r_{ds}} = \frac{0.4}{666 \text{ k}\Omega} = 0.77 \mu\text{A}$$

$$\text{Error \%} = \frac{0.77 \mu\text{A}}{20 \mu\text{A}} = \underline{\underline{3.8\%}}$$

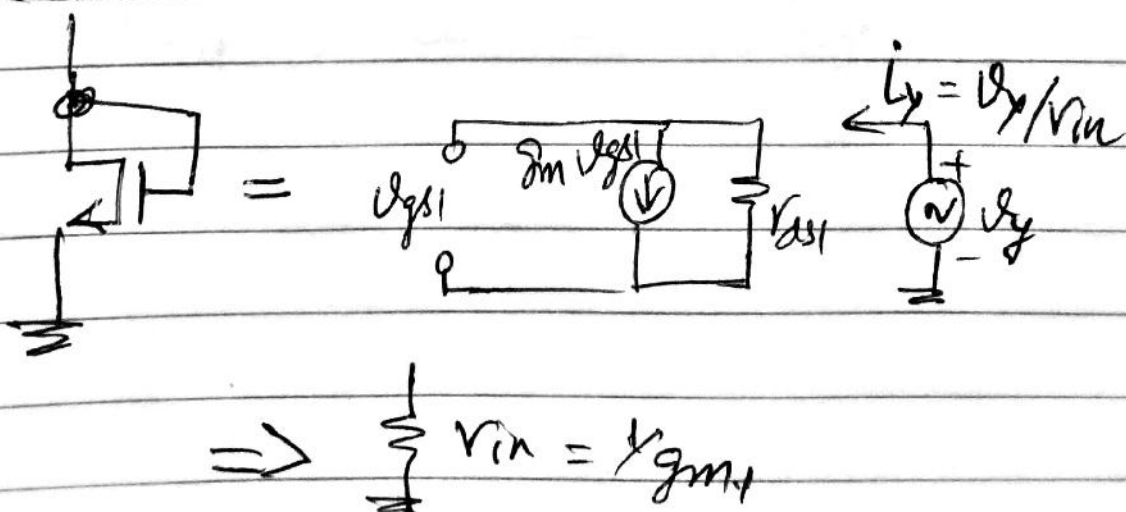Small-signal Analysis of Diode
connected Transistor



Output Impedance

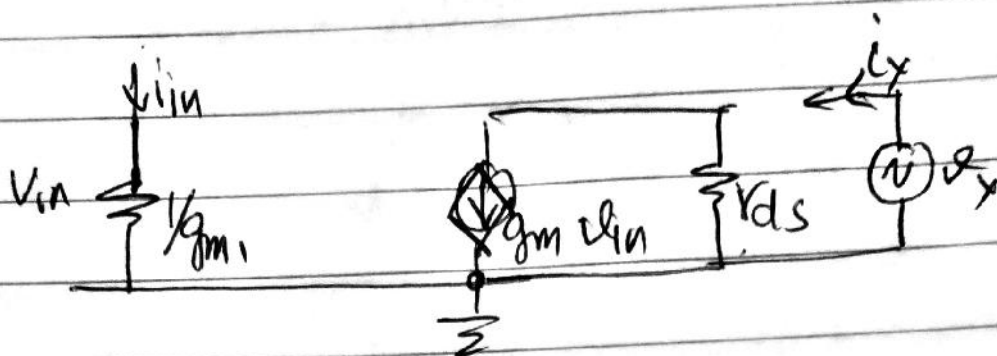

$$\boxed{Y_{out} = r_{ds}}$$

To find output impedance


* Turn off all independent sources (AC, DC) to zero.

* Apply a test voltage (v_x) to the port of interest & measure current i_x

* Impedance = v_x / i_x

Problem 3.1

0.8 μm nMOS

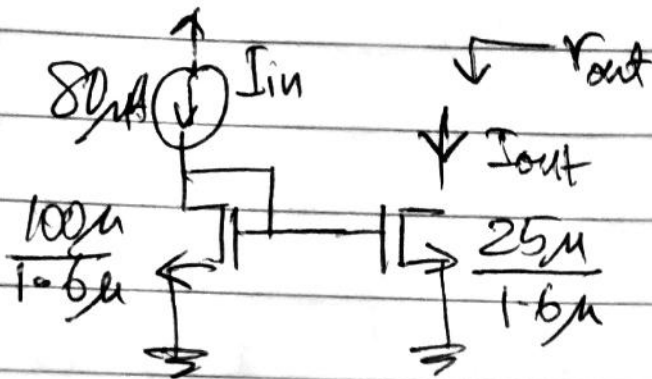

$$\mu_{\text{Lox}} = 92 \mu\text{A/V}^2$$

$$V_{\text{tn}} = 0.8 \text{ V}$$

$$\lambda \cdot L = 0.12 \mu\text{m/V}$$

Find ① nominal o/p current

② r_{out}

③ Output voltage compliance.

① Nominal o/p current = $20 \mu\text{A}$


② $r_{\text{out}} = 666 \text{ k}\Omega$

③ $V_{\text{eff}} = 0.166 \text{ V}$

} previously
calculated.

source degenerated Current Mirror:

$$M_1 = M_2$$

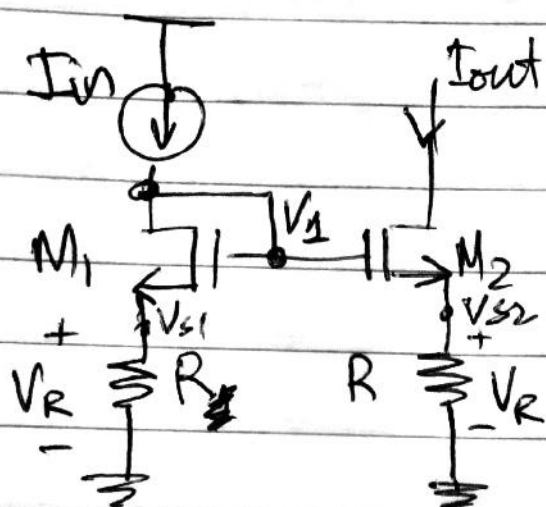

$$V_1 = I_{in} \cdot R + V_{gs1}$$

$$I_{out} = \frac{\mu_n C_{ox}}{2} \frac{W_2}{L_2} (V_1 - V_{gs2} - V_T)^2$$

$$V_1 = I_{in} \cdot R + V_{gs1}$$

$$\text{or } I_{out} = \frac{\mu_n C_{ox}}{2} \frac{W_2}{L_2} \left[(I_{in} - I_{out})R + V_{gs1} - V_T \right]^2$$

∴ $M_1 = M_2$, only soln is $I_{in} = I_{out}$

Another way to prove it


① If $I_{out} > I_{in} \Rightarrow V_{gs2} < V_{gs1}$
 & ∴ $I_{DS2} < I_R \leftarrow$ not possible.

② If $I_{out} < I_{in} \Rightarrow V_{gs2} > V_{gs1}$
 ∴ $I_{DS2} > I_R \leftarrow$ again not possible

$$\boxed{I_{out} = I_{in}}$$

Output Impedance: Source deg'n CM.

Neglecting g_{mb}

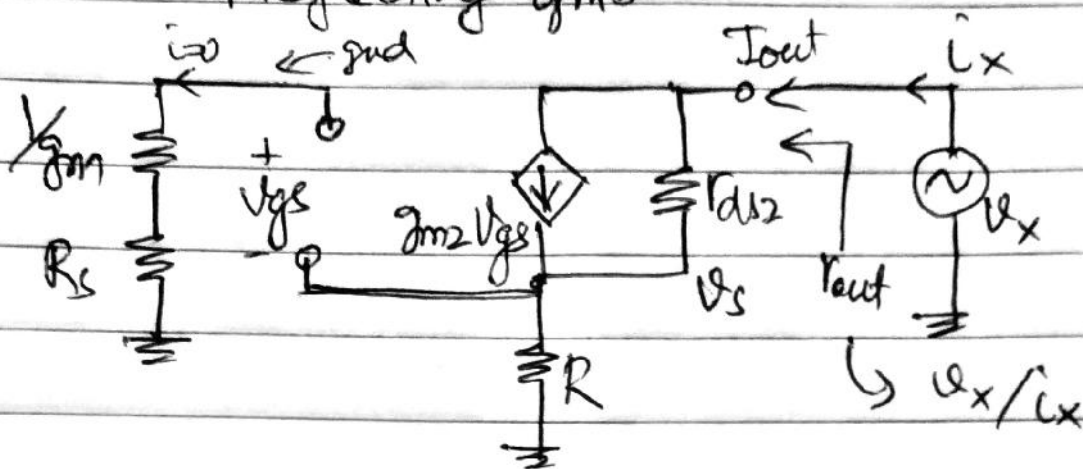

KCL @ node I_{out}

$$i_x = -g_{m2}v_s + (v_x - v_s)g_{ds2} \quad \text{--- (1)}$$

KCL @ node v_s

$$v_s = i_x \cdot R \quad \text{--- (2)}$$

On substituting (2) in (1) we get

$$r_{out} = \frac{v_x}{i_x} = r_{ds2} [1 + (g_{m2} + g_{ds2})R]$$

Typically $g_{m2} \gg g_{ds2}$

$$\therefore r_{out} \approx r_{ds2} [1 + g_{m2}R]$$