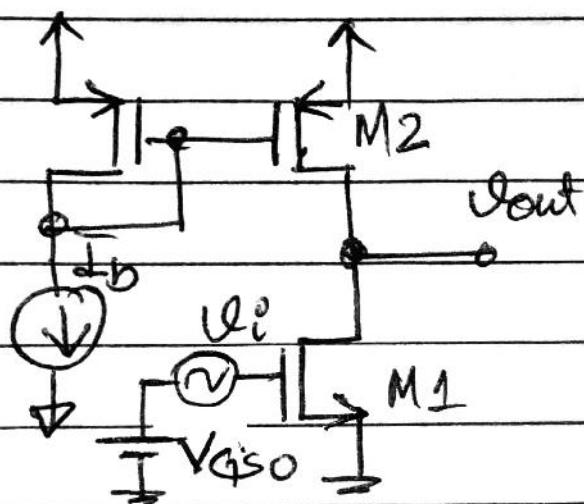


FEEDBACK

* Why feedback.

Let's look at two problems with a so-called open-loop (ie. no feedback) amplifiers eg. common-source amplifier.



Problem-1 : Gain variability.

$$\text{Gain} = \frac{V_{out}}{V_{in}} = -g_{m1} \cdot (r_{ds1} \parallel r_{ds2})$$

Both g_m & r_{ds} vary wildly over (1) process & (2) temperature since μ , V_T are strong functions of process & temperature.

Problem-2 : Distortion.

The gain, $g_m(r_{ds1} \parallel r_{ds2})$ is a small-signal approximation.

In reality, the transistor is non-linear and therefore the output will be distorted as the input signal grows in amplitude.

Let the time-varying input
 $v_i = V_m \sin \omega t$

The large-signal drain current I_{DS} can be written as

$$I_{DS1} = \frac{\mu_{n0} \epsilon_0}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

\swarrow DC bias

$$= \underbrace{\frac{\mu_{n0} \epsilon_0}{2} \frac{W}{L}}_{\beta} (V_{GS0} + 2V_m \sin \omega t - V_T)^2$$

$$= \underbrace{\beta (V_{GS0} - V_T)^2}_{\text{DC bias}} + \underbrace{\beta \cdot 2V_m \sin \omega t}_{g_m \cdot v_i} + \underbrace{\beta V_m^2 \sin^2 \omega t}_{\text{Distortion}}$$


Using trigonometric relation the distortion term can be expanded to

$$\beta' \cdot V_m^2 \sin^2 \omega t = \frac{\beta'}{2} V_m^2 (1 + \cos 2\omega t)$$

2nd harmonic distortion.

Therefore $V_{out} = \text{Gain} \cdot V_m + \underbrace{V_D}_{\text{unwanted distortion}}$

Feedback

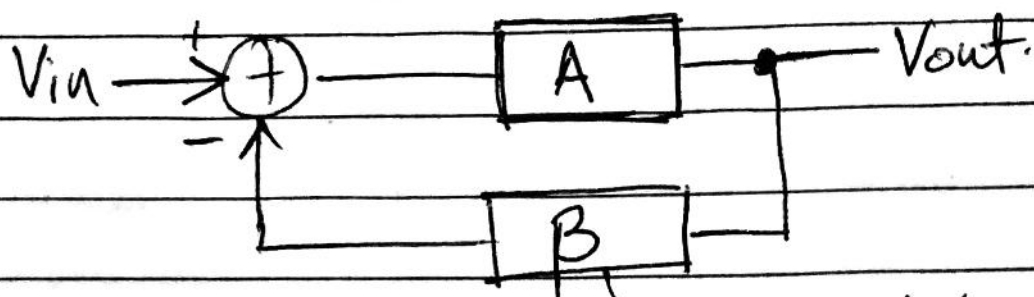

$\beta = 1/G$
where G is the
desired gain.

The idea is: Put a large gain block A in the so-called feed-forward path which can vary wildly and sample the output with accurate multiplier β which is $1/G$ the desired gain and subtract it from the input to result in $G = \frac{V_{out}}{V_{in}} = \frac{1}{\beta}$

°° $G > 1$ °° $\beta < 1$ which
easily realizable through simply
a resistor divider.

$$\frac{V_{out}}{V_{in}} = \frac{A}{1 + B \cdot A} = A_{CL} = G$$

\nwarrow \swarrow
 Loop gain = L or T closed-loop gain OR desired gain

It can be seen from the above equation that for large A

$$\frac{V_{out}}{V_{in}} \approx \frac{1}{B}$$

Gain sensitivity:

Now let's see how much $V_{out}/V_{in} = A_{CL}$ varies for variation in A.

$$\frac{dA_{CL}}{dA} = \frac{d}{dA} \left(\frac{A}{1 + BA} \right) = \frac{1}{(1 + BA)^2}$$

The gain sensitivity S_A can be defined as

$$S_A = \frac{dA_{CL}/A_{CL}}{dA/A} = \frac{1}{1 + BA} = \frac{1}{1 + L} = \frac{1}{1 + T}$$

$$\therefore \quad B \cdot A \gg 1 \Rightarrow \underline{S_A \ll 1}$$

Example

Let desired gain $A_{CL} = 10$
 $\Rightarrow \beta = 1/10$


& Let $A = 1000$

$$S_A = \frac{1}{1+100} \approx \underline{0.01}$$

Now let's say A varies by $\pm 10\%$
i.e. 1000 ± 100 (900 - 1100)

then closed-loop gain A_{CL}
varies by $0.01 \times 10\% = \underline{0.1\%}$

Op-Amp example:

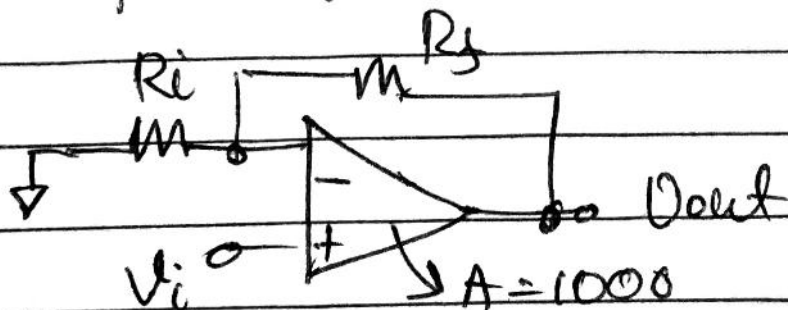


$$\text{For } \frac{V_{out}}{V_i} = 10 \quad \beta = \frac{1}{R_f/R_i} = \frac{1}{10}$$


$\Rightarrow R_f/R_i = 10 \leftarrow$ ratio of resistors
variability is low.

Feedback improving distortion

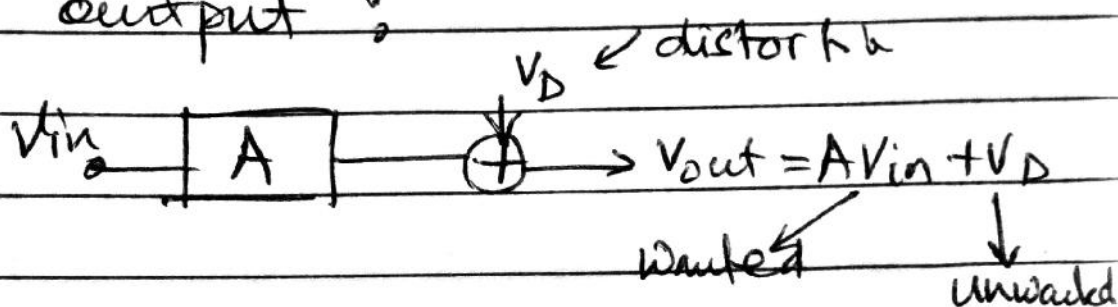The distortion can be modeled as the linear amplifier with an unwanted signal added at the output:



With feedback

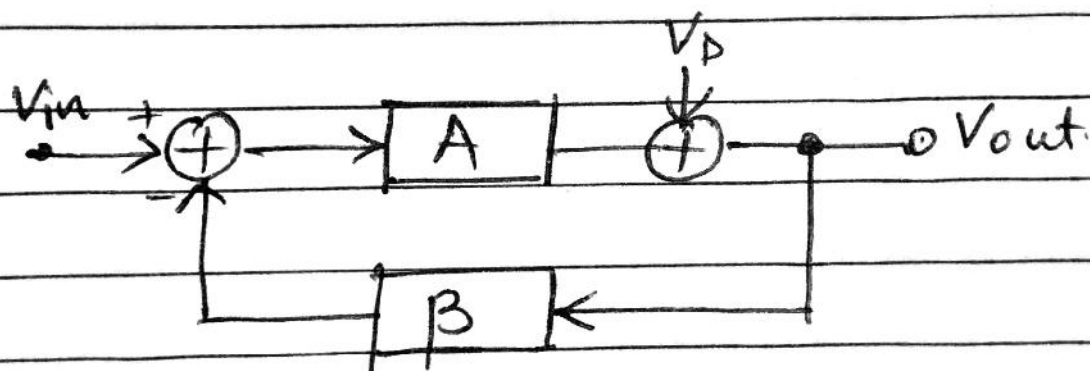


If we want to find the distortion in V_{out} :

$$\left. \frac{V_{out}}{V_D} \right|_{V_{in}=0} = \frac{1}{1 + \beta A} \approx \frac{1}{\beta A} \approx 0$$


$$V_{out} = \frac{V_{in}}{\beta} + \frac{V_D}{\beta A} \approx 0$$

Gain-Bandwidth Trade-Off.

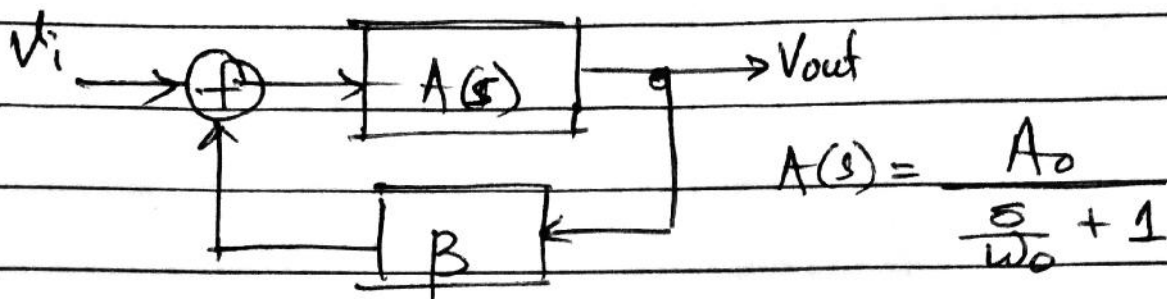

$$\frac{V_{out}}{V_{in}} = A_{cl} \approx \frac{1/B}{\frac{s}{w_0 \cdot BA} + 1}$$


↘ BW extension.

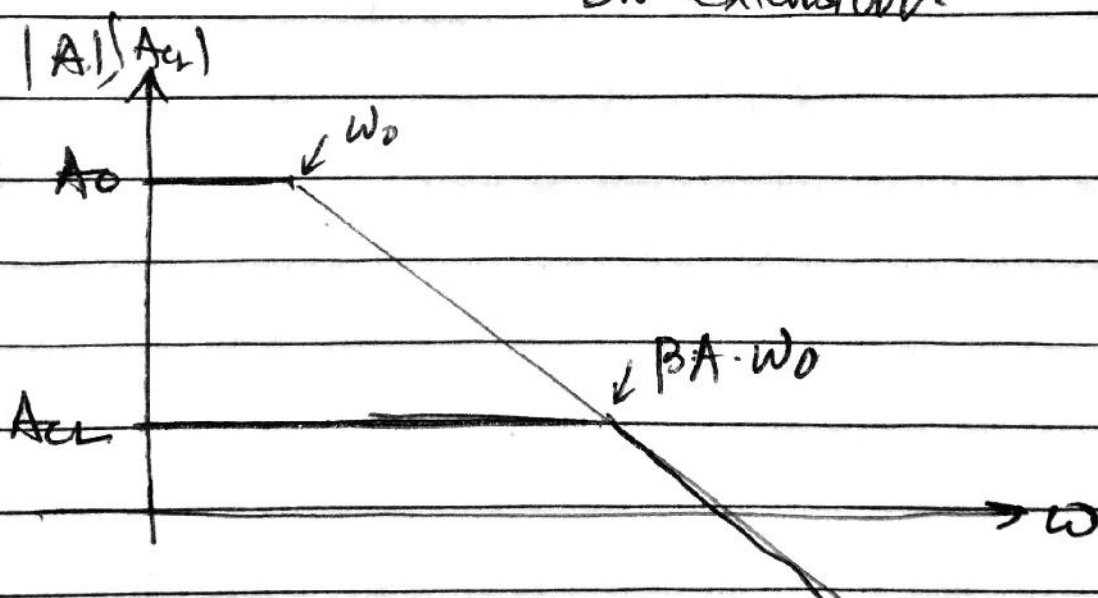

STABILITY CRITERIA.

* All poles of $A_{CL}(s) = \frac{V_{out}}{V_{in}}(s)$ should be in the left-half plane.

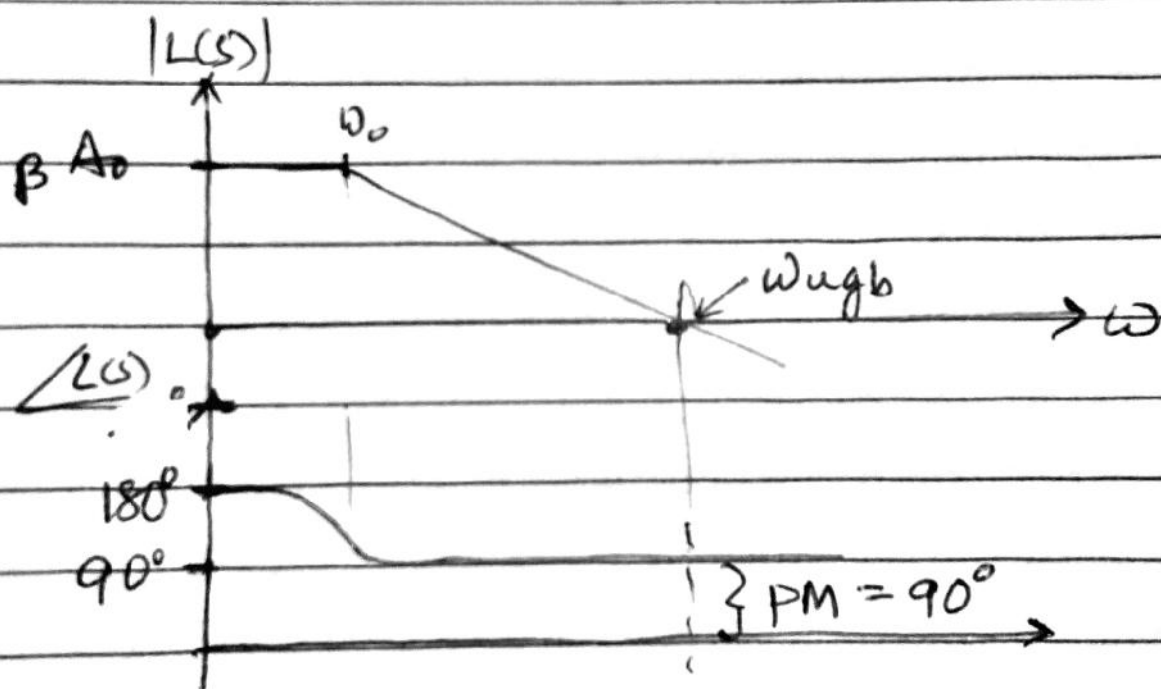* The stability criteria is evaluated easily from the Bode Plot of the loop-gain $L(s) = \beta \cdot A(s)$



Stability criteria:

① Phase Margin (PM) $> 0^\circ$ but should be typically more than 45°

$$PM = 180^\circ - \angle L(j\omega) \bigg|_{\text{at } \omega = \omega_{ugb} \text{ and } \beta A_0 = 1}$$

② Gain Margin (GM) < 0 dB
and typically desired < -10 dB.

$$GM = \text{Gain @ } \omega \text{ when } \angle L(j\omega) = 0^\circ$$