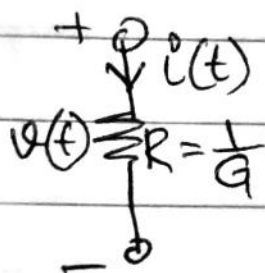


RECAP : CIRCUIT THEORY AND ANALYSIS

Circuit Elements and their constitutive relations (relating branch voltages & current)

Resistor




$$v(t) = R \cdot i(t)$$

$$i(t) = G \cdot v(t)$$

$$\text{Units: } R \rightarrow \Omega$$

$$G \rightarrow \mathcal{S} \text{ (Siemens)}$$

Capacitor

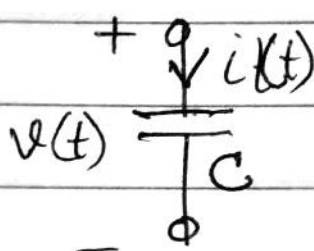


$$i(t) = C \frac{dv(t)}{dt}$$

or

$$v(t) = v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau$$

$$\text{Unit: Farad}$$

Inductor

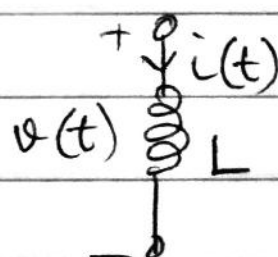


$$v(t) = L \frac{di(t)}{dt}$$

or

$$i(t) = i(0) + \frac{1}{L} \int_0^t v(\tau) d\tau$$

$$\text{Unit: Henry}$$

Ideal Independent Voltage source

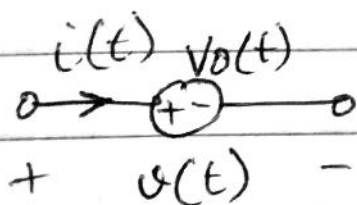


$$v(t) = v_0(t)$$

independent of $i(t)$

Units: Volts

Ideal Independent Current source

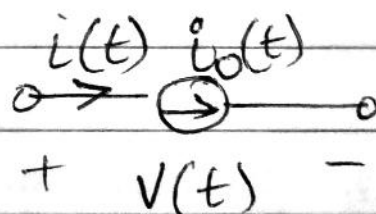

$$i(t) = i_0(t)$$

independent of $v(t)$

Units: Amperes


Dependent sources

— Used mostly in modeling active devices & simulation testbenches.

① Voltage-Controlled Voltage source (VCVS)

✓ Eg.

Op-Amp modeled with a VCVS

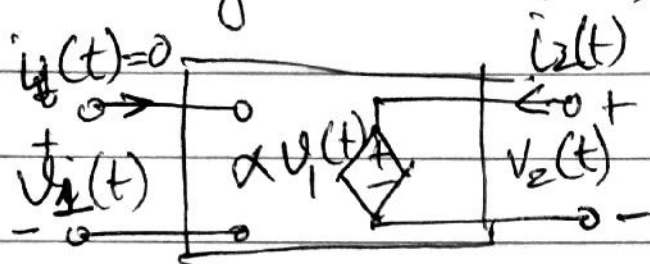


$$v_2(t) = \alpha v_1(t)$$

independent of $i_2(t)$

$\alpha \rightarrow$ Voltage gain (Unitless)

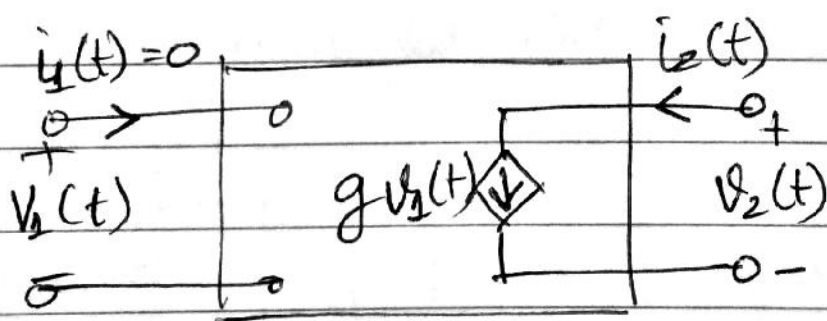② Voltage-controlled current source (VCCS)




$$i_2(t) = g \cdot v_1(t) \text{ independent of } v_2(t)$$

$g \rightarrow$ transconductance. (Unit: siemens)

Eg. Transistor modeled with a VCCS

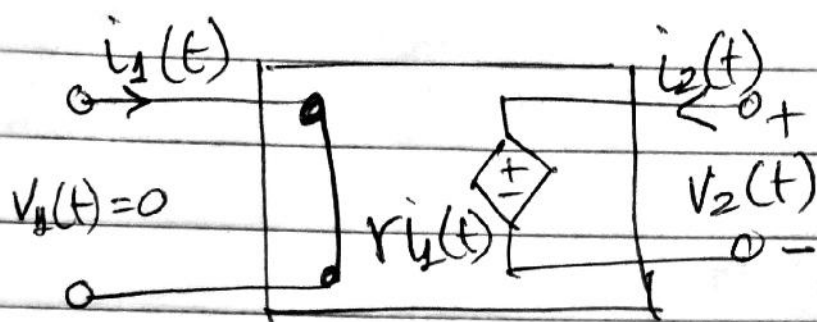③ Current-controlled Voltage source (CCVS)




$$V_2(t) = r \cdot i_1(t) \text{ independent of } i_2(t)$$

$r \rightarrow$ transimpedance. (Unit: Ω)

Eg: Transimpedance amplifier modeled with CCVS

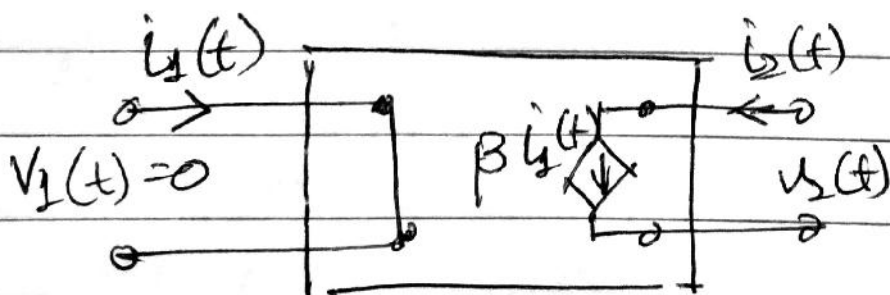④ Current-controlled Current source (CCCS)




$$i_2(t) = \beta i_1(t) \text{ independent of } V_2(t)$$

$\beta \rightarrow$ current gain (Unitless)

Eg: modeling current amplifier.

Ideal Op-Amp.

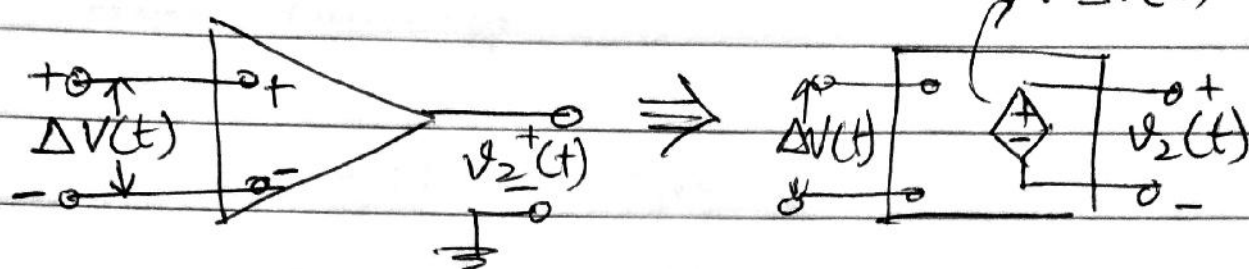

The linear circuit elements and their network satisfy

SUPERPOSITION (LINEARITY) PRINCIPLE

If $i'(t)$ & $v'(t)$ satisfy the constitutive relation of an element or system, and $i''(t)$ & $v''(t)$ also satisfy the same then, the element or the system is said to be linear if.

$i(t) = a i'(t) + b i''(t)$ & $v(t) = a v'(t) + b v''(t)$ also satisfy the constitutive relation for any a & b .

~~Lin~~

linear circuits & systems
also satisfy

TIME-INVARIANCE PRINCIPLE

If $i(t)$ & $v(t)$ satisfy the
constitutive relations, then
 $i(t-T)$ & $v(t-T)$ also satisfies
for any value of T


Circuits composed entirely of linear
time-invariant elements (except independent
sources), form Linear Time-Invariant (LTI)
systems.

ANALYTICAL TOOLS FOR ANALYZING, UNDERSTANDING & DESIGNING LTI SYSTEMS.

KIRCHOFF'S LAWS.

KIRCHOFF'S CURRENT LAW (KCL):

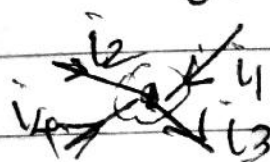Algebraic sum of the currents
entering/leaving a circuit node is zero.




$$i_1 + i_2 - i_3 - i_4 = 0$$

$$\sum i_i = 0$$

KIRCHOFF'S VOLTAGE LAW (KVL)

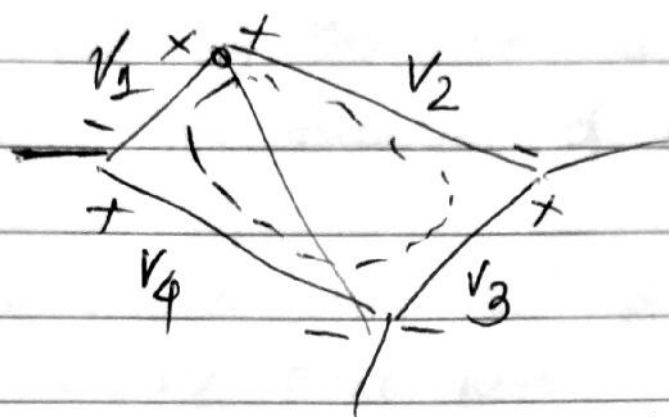Algebraic sum of the directed voltage drops around any circuit mesh is zero.



$$\sum V_k = 0 \Rightarrow V_1 - V_2 - V_3 + V_4 = 0$$


NOTE: KCL & KVL are derived from Maxwell's equations with the assumption that there is no radiation.

Together, Kirchhoff's laws & the constitutive relations provide a set of $2N$ independent equations for N voltages & N currents associated with N branches of the circuit.

Several techniques are available for reducing the number of unknowns.

The first such procedure is

KCL, KVL Example

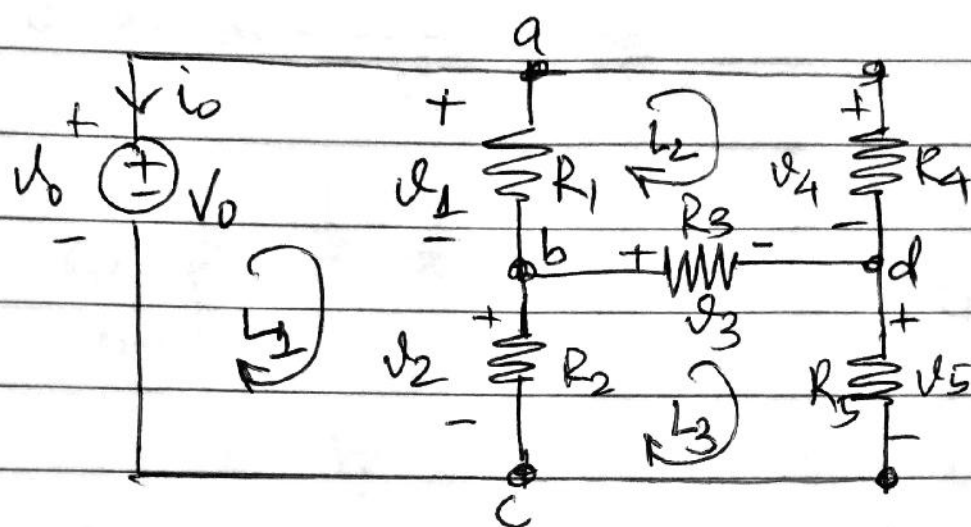

$v_0 \dots v_5, i_0 \dots i_5 \leftarrow 12$ unknowns

① Element relationships (v, i)

$$v_0 = v_0, \quad v_3 = i_3 R_3, \quad v_1 = i_1 R_1$$

$$v_4 = i_4 R_4, \quad v_2 = i_2 R_2, \quad v_5 = i_5 R_5$$

— 6 eqns

② KCL at the nodes

redundant

$$a: i_0 + i_1 + i_4 = 0; \quad b: i_2 + i_3 - i_1 = 0$$

$$d: i_5 - i_3 - i_4 = 0; \quad c: -i_0 - i_2 - i_5 = 0$$

— 3 independent equations.

③ KVL for loops:

$$L1: -v_0 + v_1 + v_2 = 0; \quad L2: v_1 + v_3 - v_4 = 0$$

$$L3: v_3 + v_5 - v_2 = 0 \leftarrow 3 \text{ independent eqns}$$

12 eqns, 12 unknowns, solve UGLY! (??)

NODE EQUATIONS PROCEDURE

1) Pick a reference node.

The resulting eqns. will be simplest if the chosen node is one ~~of the~~ that is common to largest number of branches.


2) Assign a node voltage variable to every other node, except the only one of two nodes connected by an ideal voltage source (independent or dependent) need be assigned a node voltage variable.

3) Write KCL for all assigned node using the constitutive relations.

(If one or more ideal voltage sources are connected, write KCL enclosing the voltage source.)

The node equations lead to as many equations as there is unknown which is very much less than $2 \times$ the number of branches.

EXAMPLE

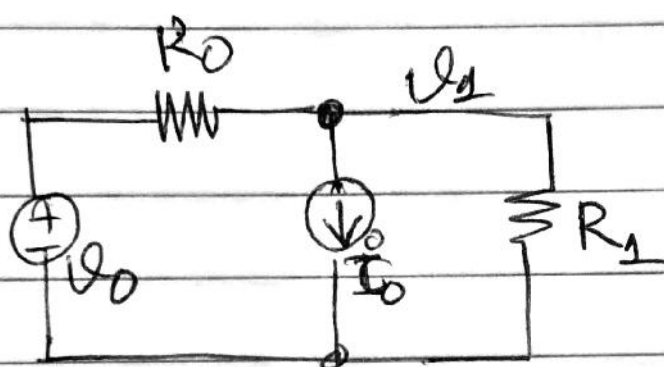

- 1) Choose this to be the reference node since most elements share this node.
- 2) Name all the voltage nodes.
Only v_1 since the other node is in series with an independent source.
- 3) Write KCL for node v_1 :

$$(v_1 - v_0)/R_0 + i_0 + \frac{v_1}{R_1} = 0$$

$$\Rightarrow V_1 = \frac{R_1}{R_1 + R_0} (V_0 - i_0 R_0)$$

Using super position:

① $i_0 = 0$ [open]

$$V_1' = \frac{R_1}{R_1 + R_0} V_0 \quad \text{--- (1)}$$

② $V_0 = 0$ [short]

$$V_1'' = -\frac{R_1 \cdot R_0}{R_1 + R_0} i_0 \quad \text{--- (2)}$$

By super position, ~~we~~ $V_1 = V_1'' + V_1'$

$$\Rightarrow \boxed{V_1 = \frac{R_1}{R_1 + R_0} (V_0 - i_0 R_0)}$$

Side Note:

Simplification Methods:


$$(1) \quad \begin{array}{c} R_1 \quad R_2 \quad \dots \quad R_N \\ \text{---} \text{---} \text{---} \text{---} \end{array} \Leftrightarrow \begin{array}{c} R_1 + R_2 + \dots + R_N \\ \text{---} \end{array}$$

$$(2) \quad \begin{array}{c} \text{---} \\ | \\ G_1 \\ | \\ \text{---} \end{array} \begin{array}{c} \text{---} \\ | \\ G_2 \\ | \\ \text{---} \end{array} \begin{array}{c} \text{---} \\ | \\ \vdots \\ | \\ \text{---} \end{array} \begin{array}{c} \text{---} \\ | \\ G_N \\ | \\ \text{---} \end{array} \Leftrightarrow \begin{array}{c} \text{---} \\ | \\ G_1 + G_2 + \dots + G_N \\ | \\ \text{---} \end{array}$$

$G_i = \frac{1}{R_i}$

$$(3) \quad \begin{array}{c} V_1 \quad V_2 \\ \text{---} \oplus \text{---} \oplus \text{---} \end{array} \Leftrightarrow \begin{array}{c} V_1 + V_2 \\ \text{---} \oplus \text{---} \end{array}$$

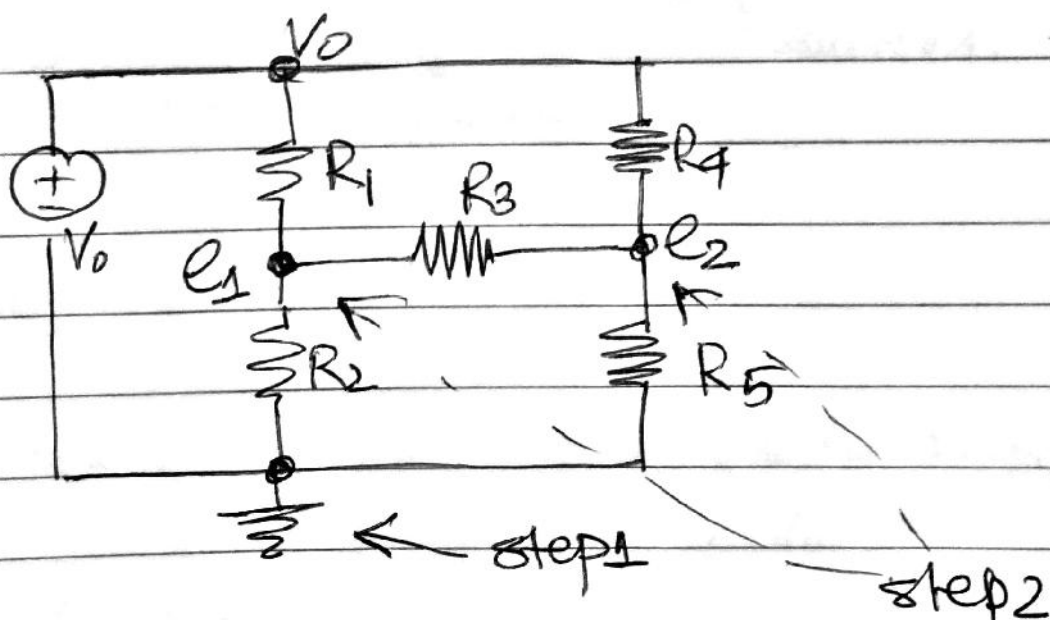SOLVE PREVIOUS EXAMPLE USING NODE METHOD:



KCL @ e_1 :

$$(e_1 - V_0)G_1 + (e_1 - e_2)G_3 + e_1 G_2 = 0$$

KCL @ e_2 :

$$(e_2 - e_1)G_3 + (e_2 - V_0)G_4 + e_2 G_5 = 0$$

Moving constants to RHS & collecting unknowns :

$$\begin{aligned}(G_1 + G_2 + G_3) \cdot e_1 - G_3 \cdot e_2 &= G_1 \cdot V_0 \\ -G_3 \cdot e_1 + (G_3 + G_4 + G_5) \cdot e_2 &= G_4 \cdot V_0\end{aligned}$$

In matrix form:

$$\begin{bmatrix} G_1 + G_2 + G_3 & -G_3 \\ -G_3 & G_3 + G_4 + G_5 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} G_1 V_0 \\ G_4 V_0 \end{bmatrix}$$

$$G \cdot \vec{e} = \vec{V}$$

Conductance matrix unknown sources.



Solve : $\vec{e} = G^{-1} \cdot \vec{V}$

Exercise : $G_1, G_5 = 1/8.2k$, $G_2, G_4 = 1/3.9k$
 $G_3 = 1/1.5k$, $V_0 = 3V$

Find e_1, e_2

Solve above using python.


THEVENIN METHOD

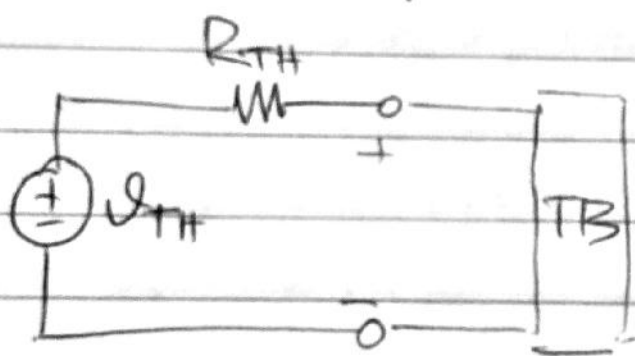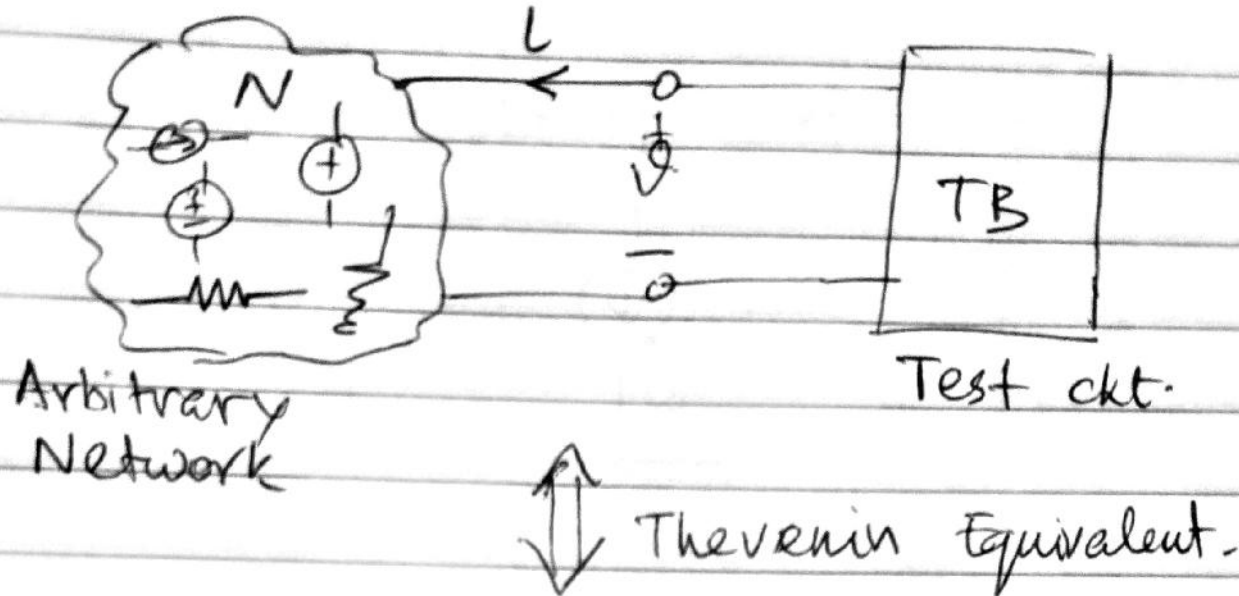

Method :

- ① V_{TH} is the open ckt. voltage at the two terminals.
- ② R_{TH} is the impedance of the two terminals when all independent sources inside the network is zero i.e. all voltage sources short & all current sources open.


Example

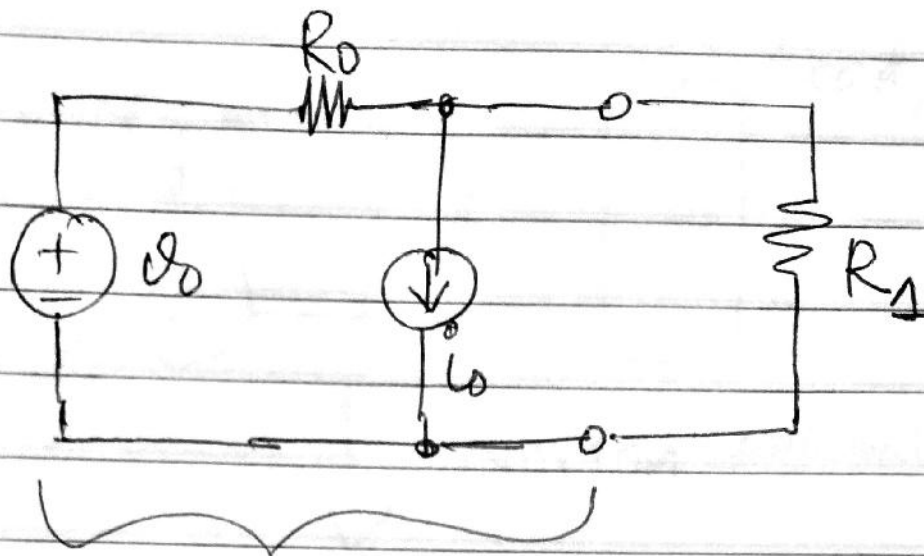

Thevenin equivalent.



- ① V_{TH} : by superposition
 $V_{TH} = V_0 - I_0 R_0$.

- ② $R_{TH} = R_0$

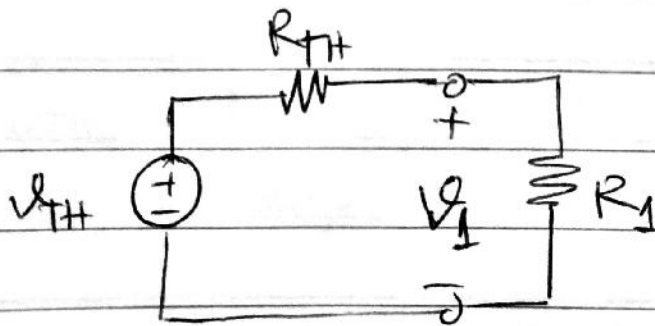

$$V_1 = \frac{R_1}{R_1 + R_{TH}} V_{TH} = \frac{R_1}{R_1 + R_0} (V_0 - I_0 R_0)$$

NORTON METHOD

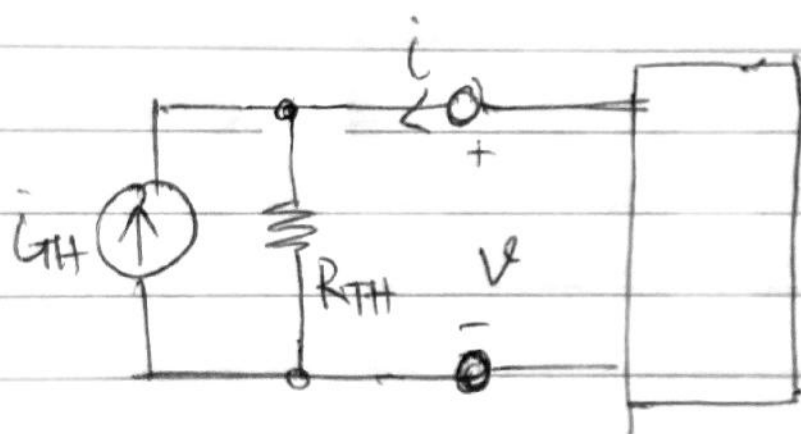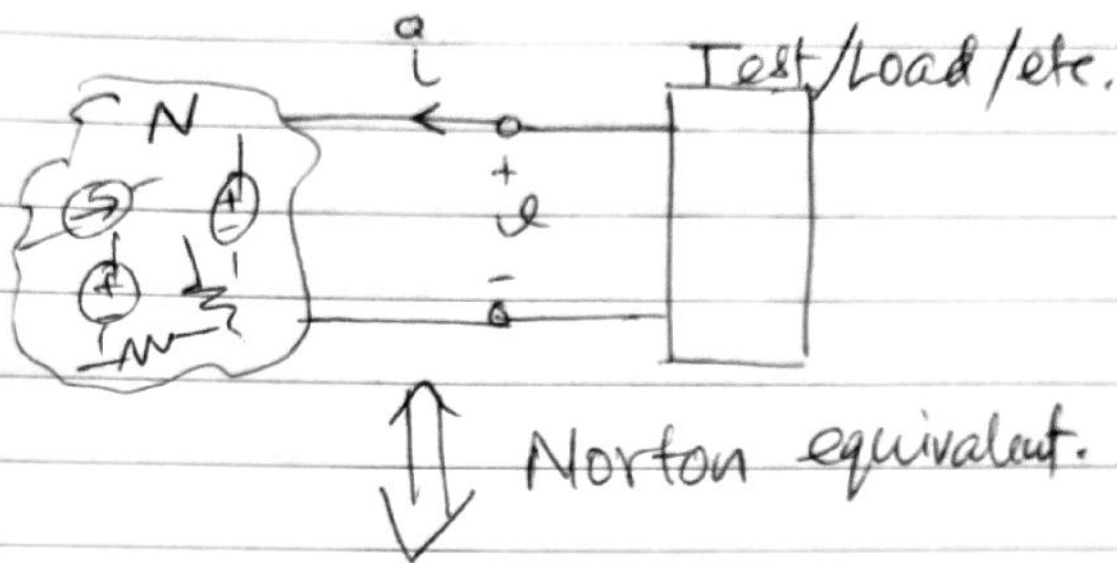

Method:


- ① i_{TH} : Find the short-circuit current by shorting the two terminals.
- ② R_{TH} : Same method as Thevenin

~~Answer~~


ANALYSIS OF NON-LINEAR CKTS.

Non-linear elements:

Diode

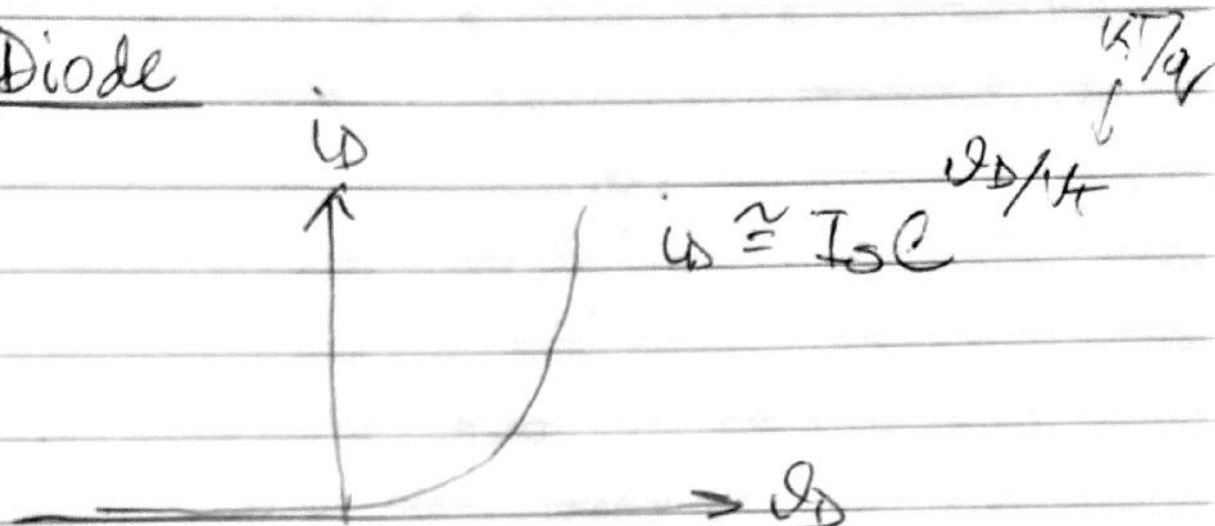


Ideal switch

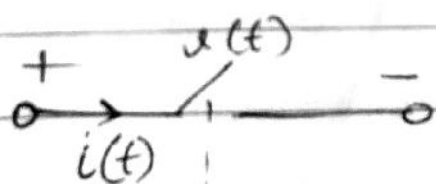


control \leftarrow independent $f(t)$

$i(t) = 0$: open state

$v(t) = 0$: close state

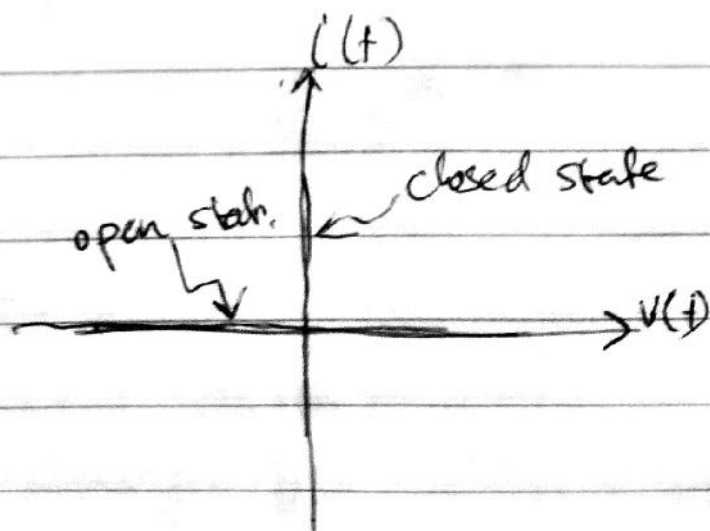

Analytical solution

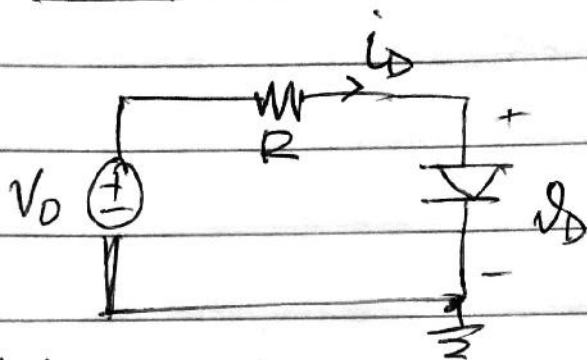


Node equation

$$\frac{V_0 - v_D}{R} - I_0 \cdot e^{v_D/V_T} = 0$$

This equation has to be solved iteratively. Not very insightful.

Graphical method

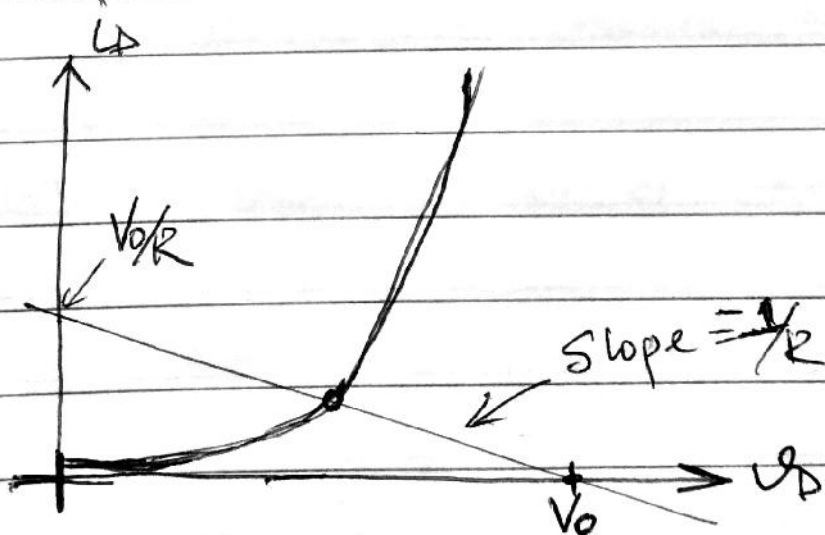


Incremental Analysis

To be covered during MOS small-signal modeling. Do Python Problem

Using Linear Analysis Toolbox to solve non-linear problems.

Example:

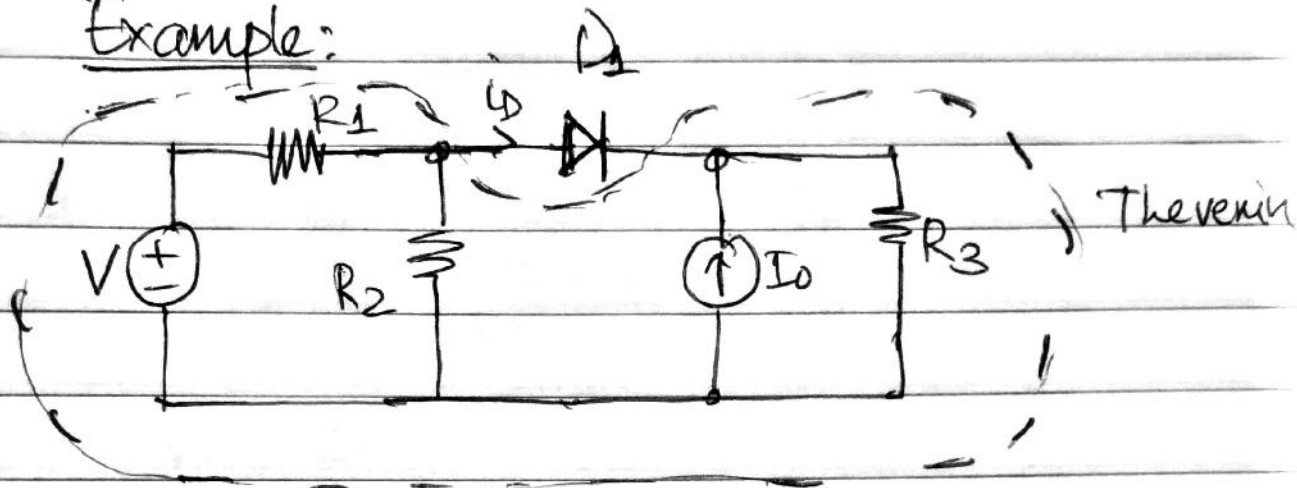

* Node analysis cannot be used since
a. non-linear element is present.


→ Thevenin/Norton equivalent of
the ckt. enclosed inside the
dotted circle.

Which one Norton or Thevenin?


→ Since we have a previous
example for a way to solve
it is, we do a Thevenin's
equivalent.

For V_{TH} (by super position) |_|_|_|

① $I_0 = 0$

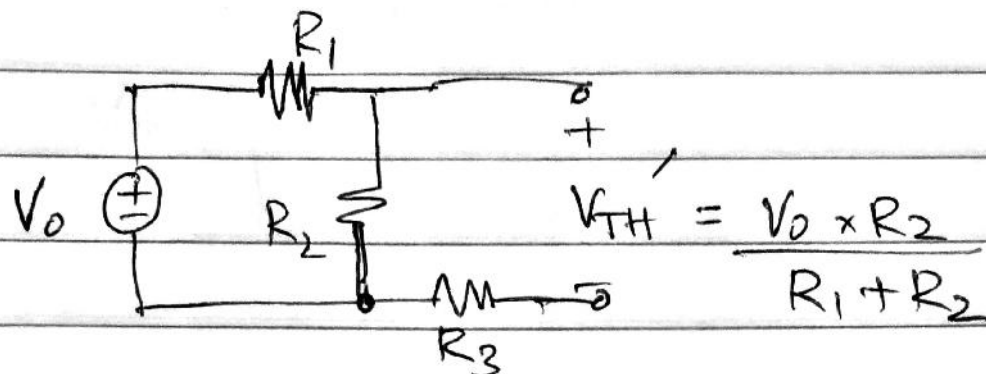


② $V_0 = 0$

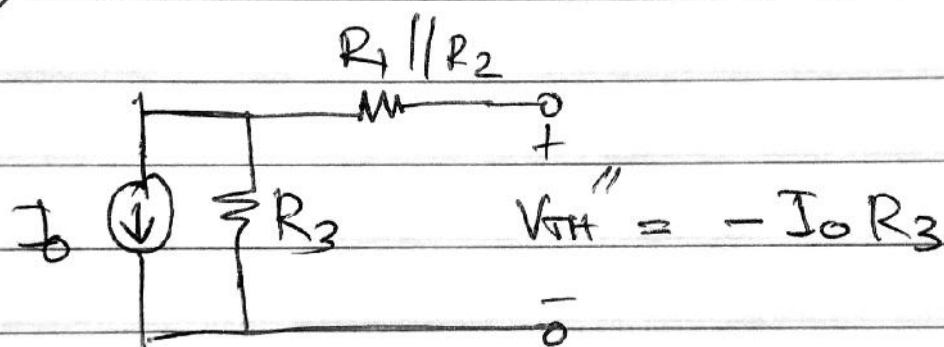

$V_{TH} = \frac{V_0 \times R_2}{R_1 + R_2} - I_0 R_3$

R_{TH}

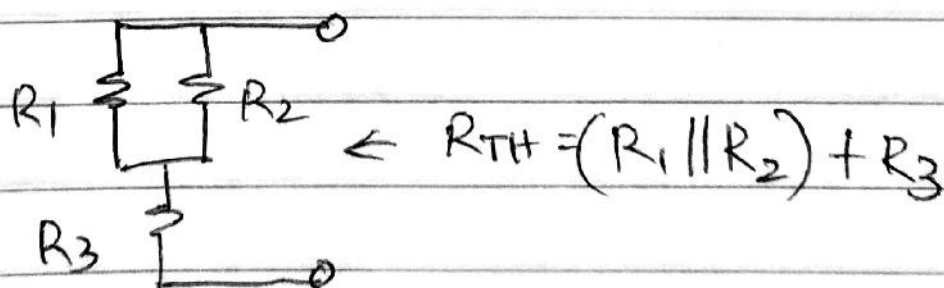

Simplified ckt.

