

# SMALL-SIGNAL MODELING

## Incremental Analysis

$$I_D = f(V_D) \leftarrow \text{Non-linear}$$

To linearize, take Taylor series of

$$f(V_D + v_d) = I_D + i_d$$

neglect  
higher-order  
terms

$$= f(V_D) + \left. \frac{\partial f(v_d)}{\partial v_d} \right|_{V_D} \times v_d + \dots$$

or

$$i_d = \underbrace{\left. \frac{\partial f(v_d)}{\partial v_d} \right|_{V_D}}_{\text{Linear term}} \times v_d$$

## SMALL-SIGNAL MODEL OF DIODE


$$\begin{aligned}
 I_D &= I_S \cdot e^{(V_D + v_d)/V_T} = I_S \cdot e^{V_D/V_T} \cdot e^{v_d/V_T} \\
 &= I_D \cdot e^{v_d/V_T} \quad \text{Taylor}
 \end{aligned}$$

Taylor series of  $e^x = 1 + x + \frac{x^2}{2!} + \dots$

for  $|x| < 1$


$$\therefore I_D \approx I_D + i_d = I_D + \frac{I_D}{V_T} \cdot v_d$$
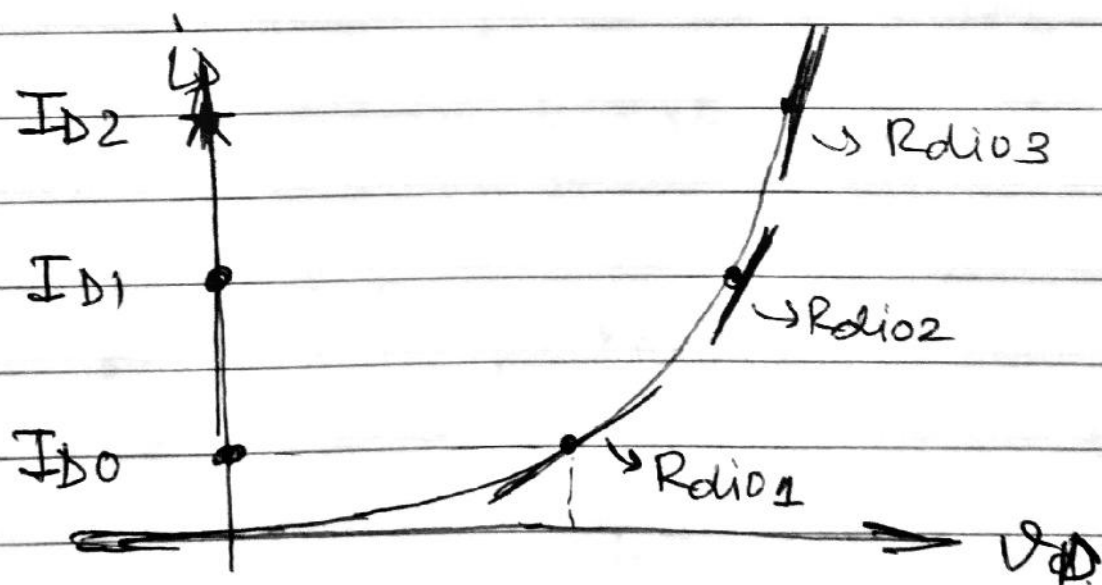
$$\therefore i_d \approx \frac{v_d}{V_T/I_D} \rightarrow R_{dio}$$




# MOS Small-Signal Model.

## Transconductance ( $g_m$ )

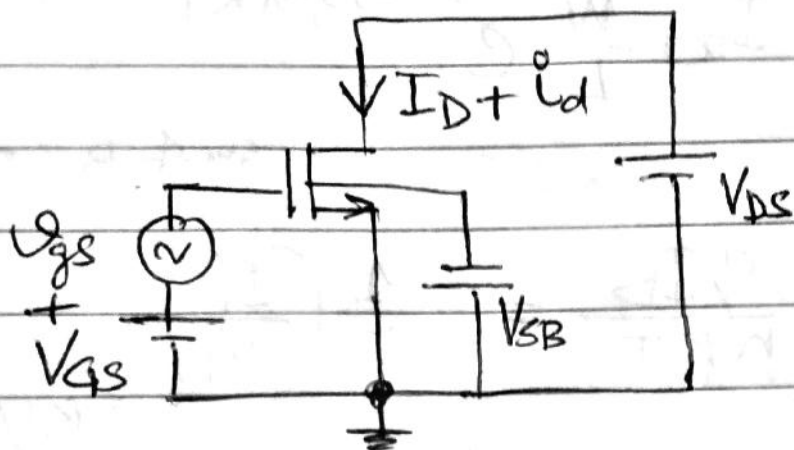

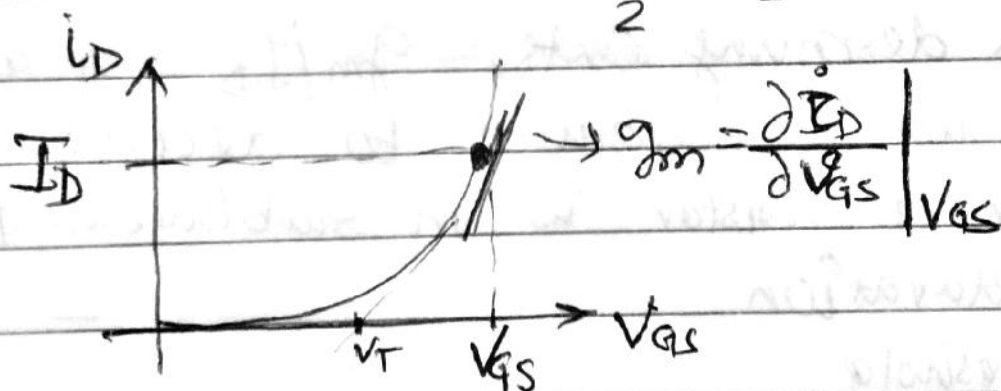Saturation :  $I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{th})^2$



$$g_m = \mu_n C_{ox} \frac{W}{L} V_{eff}$$

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

Useful for analysis when  $W/L$ ,  $I_D$  or  $V_{eff}$  is known.

$$g_m = \frac{2 I_D}{V_{eff}}$$

← Most useful for design since it separates  $I_D$  & headroom ( $V_{eff}$ )

For subthreshold region:

$$I_D = I_{D0} \frac{W}{L} e^{qV_{GS}/nKT}$$

$$g_m = \frac{qI_D}{nKT} = \frac{1}{n} \left( \frac{I_D}{V_T} \right)$$

$\swarrow$   $g_m$  of BJT       $\searrow$   $RT/q$

$$n = \frac{C_{ox} + C_{j0}}{C_{ox}} \approx 1.5$$

When designing ckts,  $g_m/I_D$  is a very useful parameter to decide if a transistor is in subthreshold or saturation

Subthreshold

$$g_m/I_D = \frac{1}{n \cdot V_T} \approx \frac{1}{1.5 \times 0.025} = 26$$

Using Inversion co-efficient -  $IC = I_D/I_S$


| IC        | 0.1 | 0.5 | 1.0 | 5.0 | 10.0 | 20.0 |
|-----------|-----|-----|-----|-----|------|------|
| $g_m/I_D$ | 28  | 22  | 19  | 11  | 8    | 6    |

deep subthreshold

moderate inversion

deep saturation

## Output Impedance

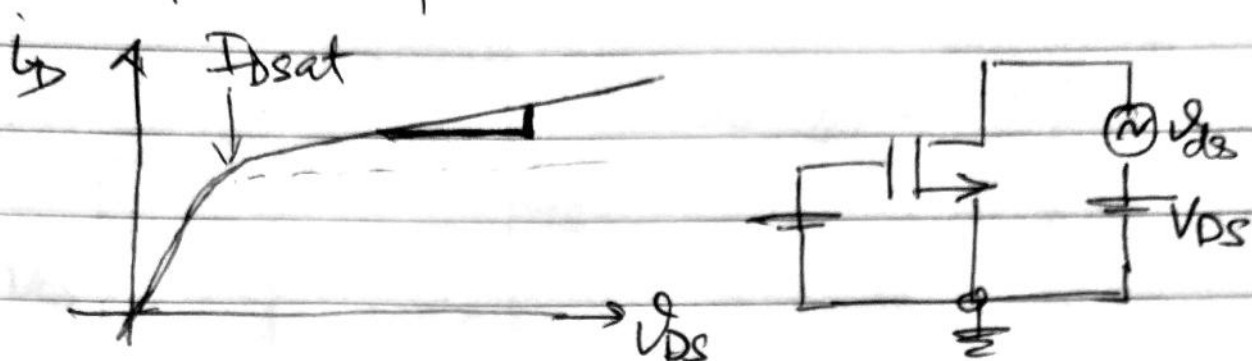


$$I_D = I_{Dsat} \cdot [1 + \lambda(V_{DS} - V_{eff})]$$

$$g_{ds} = \frac{1}{r_{ds}} = \left. \frac{\partial I_{DS}}{\partial V_{DS}} \right|_{V_{DS} = V_{DS0}}$$

$$= \lambda I_{Dsat} \approx \lambda I_D$$

$$\therefore \boxed{r_{ds} \approx \frac{1}{\lambda I_D}}$$
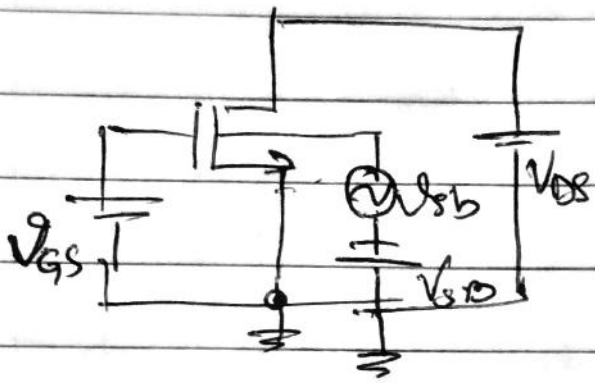
## Substrate transconductance ( $g_s, g_{mb}$ )




$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_T(V_{DS}))^2$$

$$g_{mb}' = \left. \frac{\partial I_D}{\partial V_{SB}} \right|_{V_{DS}}$$

$$g_{mb} = \frac{g_m}{2\sqrt{V_{SB}} + 2|\phi_F|}$$

# Low-frequency Small-signal Modeling

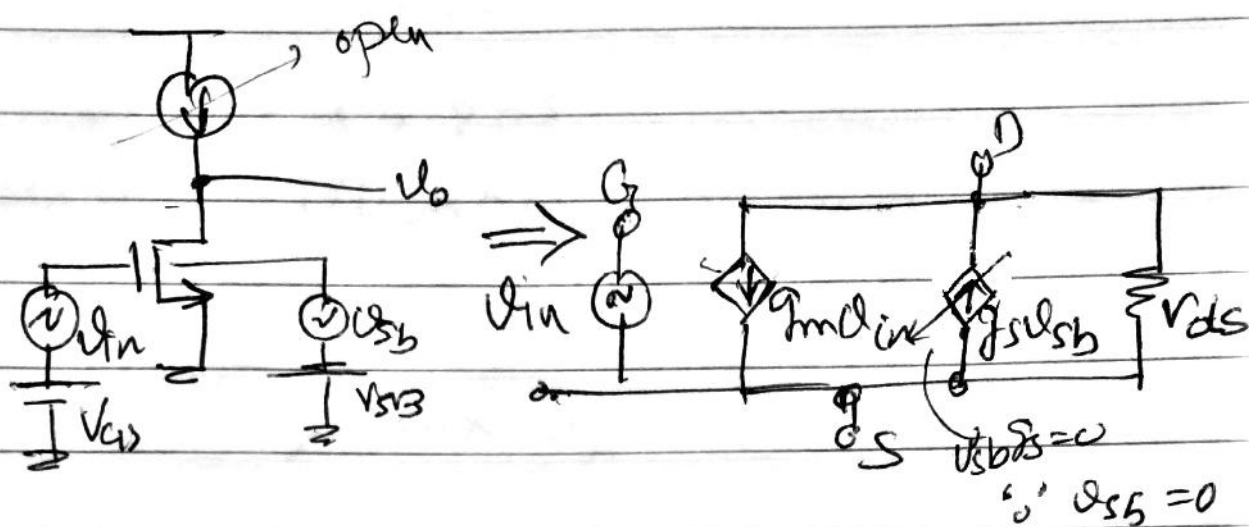

$$A_i = \frac{\partial v_o}{\partial v_i} = g_m \cdot r_{ds}$$

Problem 1.20 [Johns & Martin] 2<sup>nd</sup> Ed.

0.35  $\mu\text{m}$  NMOS to be biased with

$I_D = 350 \mu\text{A}$  with an intrinsic gain

of  $A_i = 35$ . Find  $W, L$

$$A_i = g_m \cdot r_{ds} = \frac{2 \cdot I_D}{V_{eff}} \times \frac{1}{\lambda I_D}$$

$$\Rightarrow 2/\lambda V_{eff} = 35$$

Given:  $L = 0.35 \mu\text{m}$        $\lambda \cdot L = 0.16$



$$V_{eff} = \frac{2}{\lambda \cdot 35} = 0.125 = 125 \text{ mV.}$$

From Table 1.5 p 53

$$\mu_n C_{ox} = 190 \mu\text{A/V}^2$$

$$W/L = \frac{2 \cdot I_D}{\mu_n C_{ox} V_{eff}^2} = 235 !!$$

Typically, Headroom is limited (ie,  $V_{dsat}$  is limited), a required gain decides  $L$ .

Let's say  $V_{dsat} = 200 \text{ mV}$

$$\Rightarrow L = \frac{0.16 \times 35 \times 0.2}{2} = 0.56 \mu\text{m} \quad \left[ \begin{array}{l} \lambda = \frac{2}{35 \times V_{eff}} \\ \lambda \cdot L = 0.16 \end{array} \right]$$

$$\frac{W}{L} = \frac{2 \times 350 \mu\text{A}}{190 \mu\text{A/V}^2 \times (0.2 \text{V})^2} = 92$$