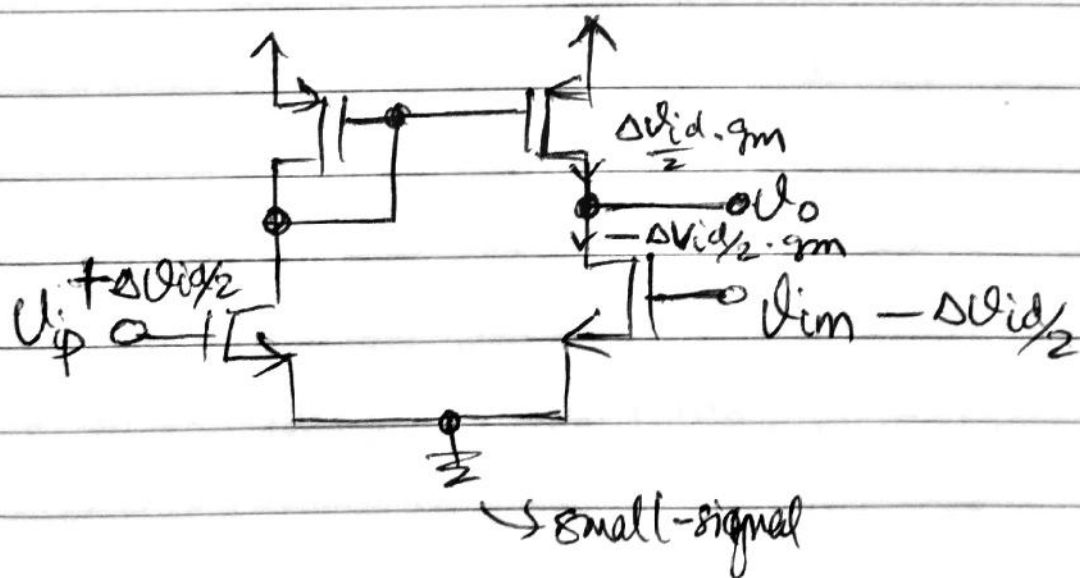


SMALL-SIGNAL GAIN OF DIFF-AMP.

Differential Gain:



Instead of drawing the entire small-signal, we can find its effective small-signal differential G_m & output impedance R_{out} & gain is $G_m \cdot R_{out}$

Since for pure diff signal, the coupled sources are constant, they look like small-signal ground.



$$\Delta I_d = \Delta V_{id} \times g_m$$

Output Impedance

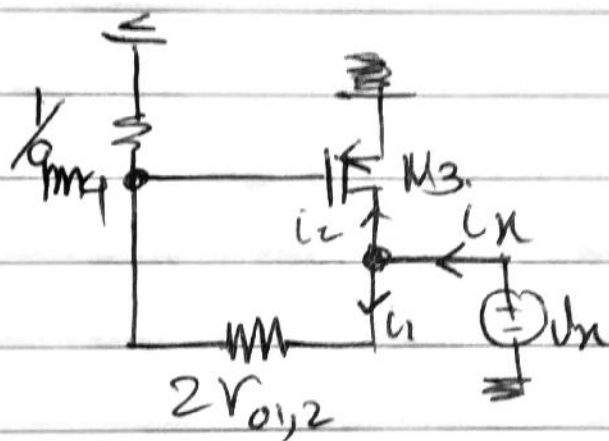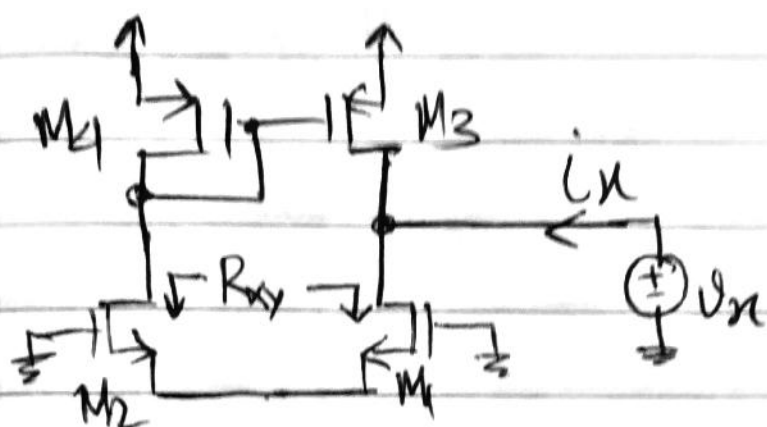

$$i_1 = \frac{V_x}{2r_{o1,2}}$$

$$i_2 = \frac{V_x}{2r_{o1,2}}$$


$$\therefore i_1 + i_2 = \frac{V_x}{r_{o1,2}}$$

$$i_n = i_1 + i_2 + i_3 = \frac{V_x}{r_{o1,2}} + \frac{V_x}{r_{o3}}$$

$$\therefore r_{out} \approx r_{o1,2} \parallel r_{o3}$$

$$|A_d| = g_{m1,2} \times (r_{o1,2} \parallel r_{o3})$$

Common-mode gain

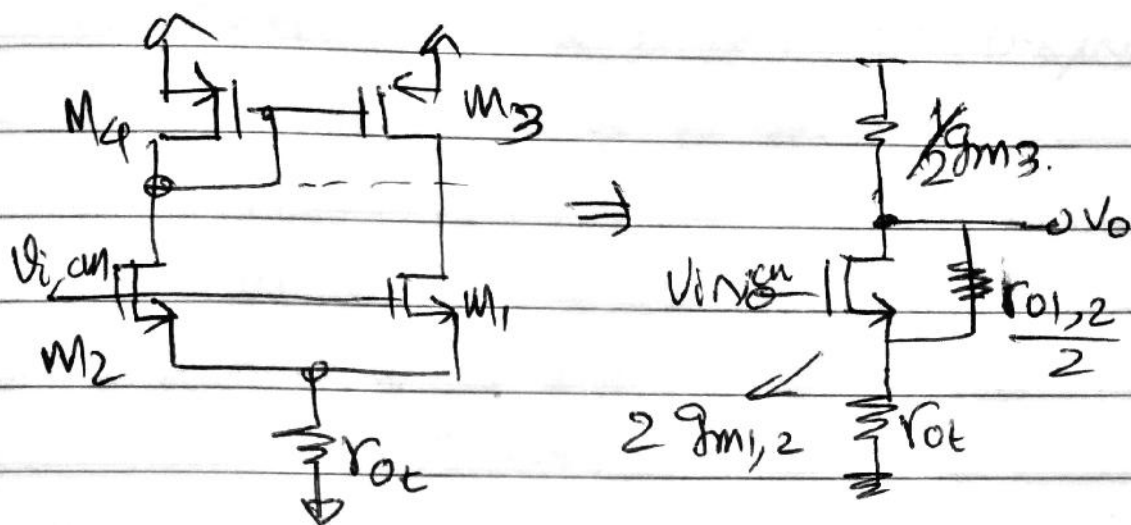

$$A_{cm} \approx \frac{-1/2 g_{m3,4}}{\frac{1}{2 g_{m1,2}} + r_{ot}} = \frac{-1}{1 + 2 g_{m1,2} \cdot r_{ot}} \frac{g_{m1,2}}{g_{m3,4}}$$

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = g_{m1,2} \cdot (r_{o1,2} \parallel r_{o3,4}) \frac{g_{m3,4} (1 + 2 g_{m1,2} r_{ot})}{g_{m1,2}}$$

$$CMRR = (1 + 2 g_{m1,2} r_{ot}) g_{m3,4} (r_{o1,2} \parallel r_{o3,4})$$